

# Analog Electronics

## Unit 9

### Unit 9. Power Supplies in analog systems


# Contents

- 1. Introduction**
- 2. Initial Stages** (Transformer, Rectifier, Filter)
- 3. Classification**
- 4. Stabilized power supplies**
- 5. Regulated power supplies**
- 6. Integrated power supplies**
- 7. Decoupling capacitors**
- 8. Non-symmetrical supply**
- 9. Consumption calculation**

# 1. Introduction

- **Electronic circuits need one or several DC voltage sources to operate correctly.**
  
- **Voltage supply with batteries:**
  - Low autonomy and high cost
  - Acceptable for low consumption
  
- **Voltage supply from the net:**
  - The most common source of primary energy source
  - Alternate sinusoidal voltage
  - Net voltage must be converted to DC voltage

# 1. Introduction

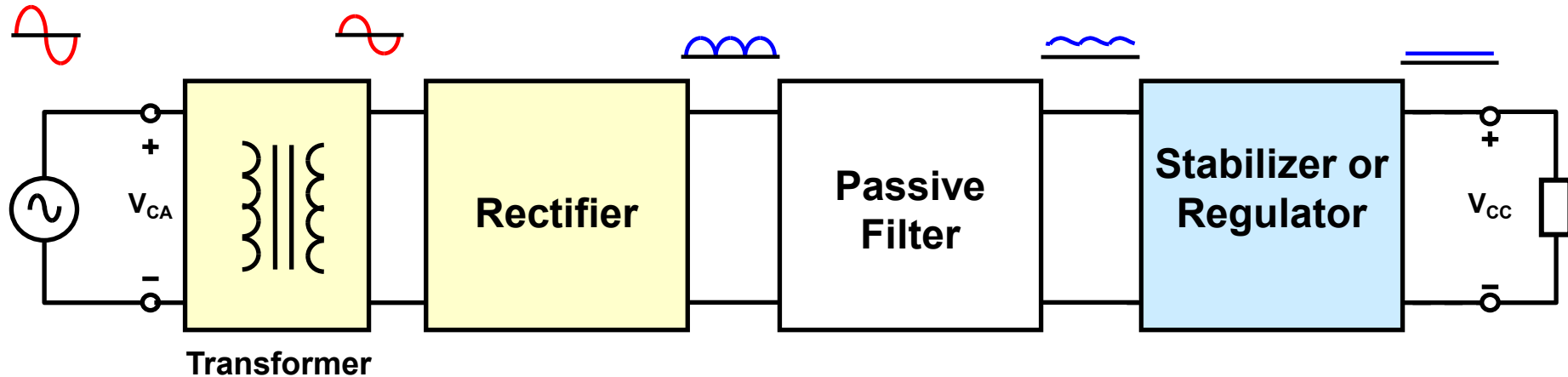

- Adapts voltage and current levels
- Stabilizes the signal

## 2. Initial stages. Transformer




### ➤ Main functions:

- Adaptation of the net voltage to the value required by the load →  $N_1 : N_2$
- Provide galvanic isolation → Protection of the user

### ➤ Several configurations depending on the choosed rectifier:

- Primary-secondary
- Transformer with tapped secondary (toma intermedia)

# 2. Initial stages. Transformer

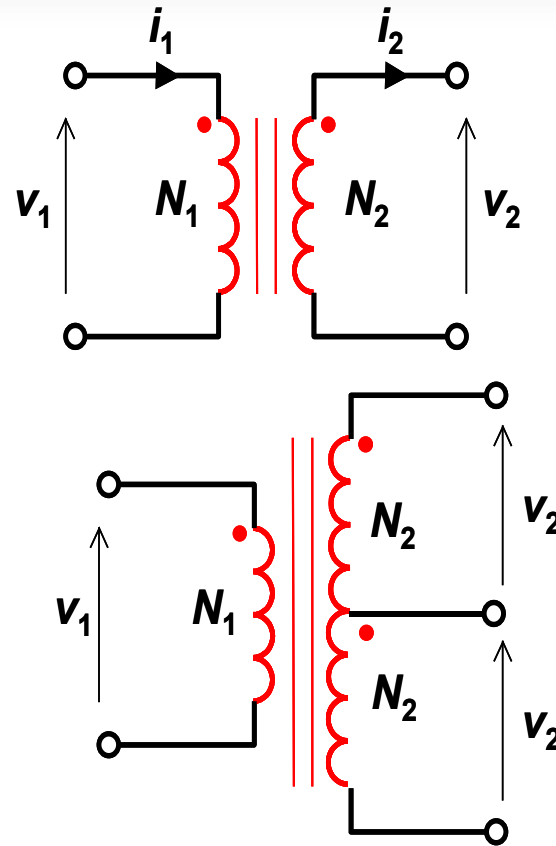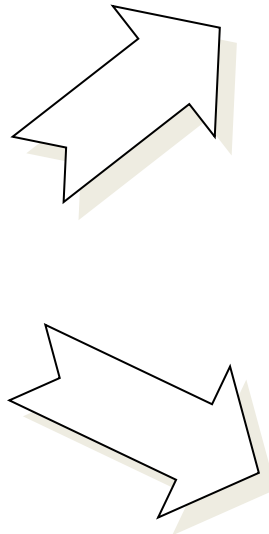
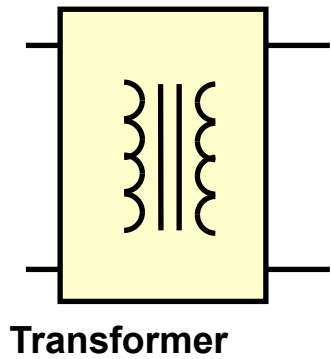


$$v_2 = \frac{N_2}{N_1} \cdot v_1$$
$$i_2 = \frac{N_1}{N_2} \cdot i_1$$

## 2. Initial stages. Rectifier

Converts the AC voltage provided by the trafo into a pulsatory unidirectional voltage with a non-zero medium value.


### Half-wave Rectifier

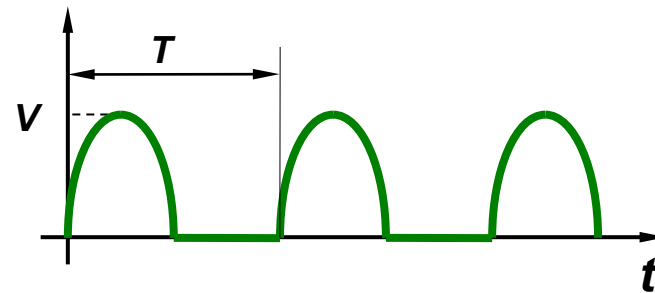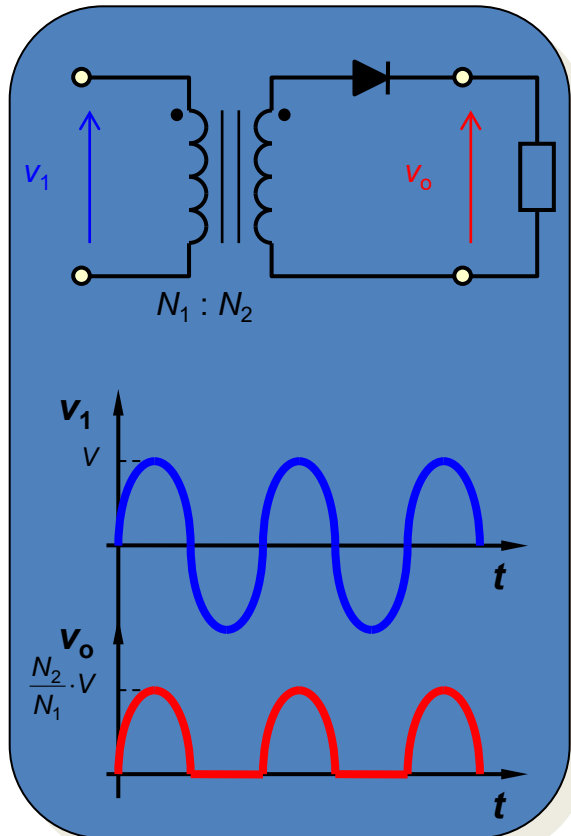

$$V_{cc} = \frac{V}{\pi}$$

## 2. Initial stages. Rectifier

### Full-wave Rectifier: Diodes bridge.

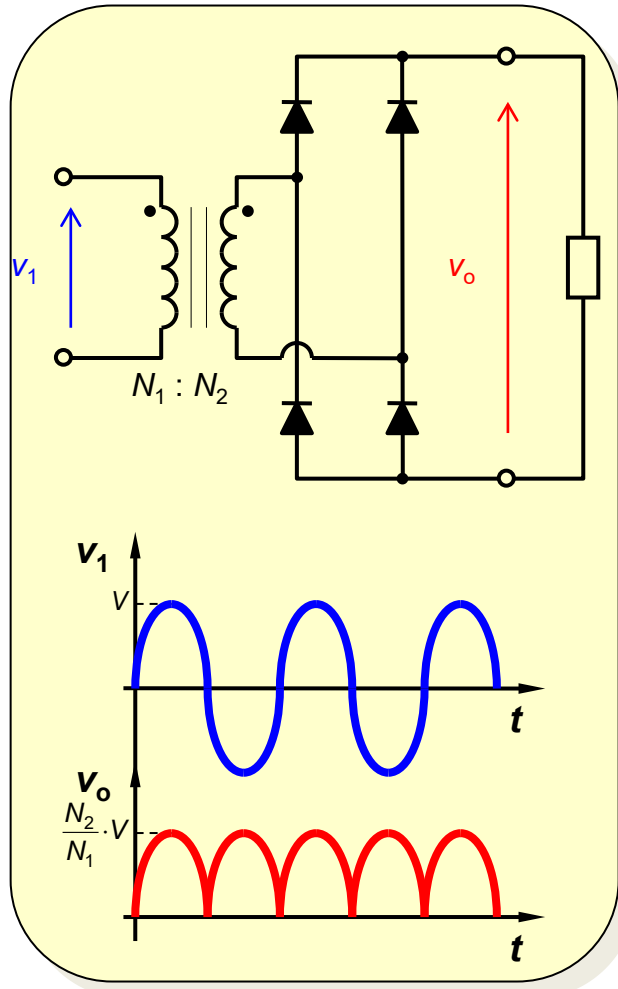


- During each hemicycle 2 diodes conduct simultaneously.
- Each diode supports an inverse voltage of the maximum voltage value of the secondary.
- This configuration is the most common.




## 2. Initial stages. Rectifier
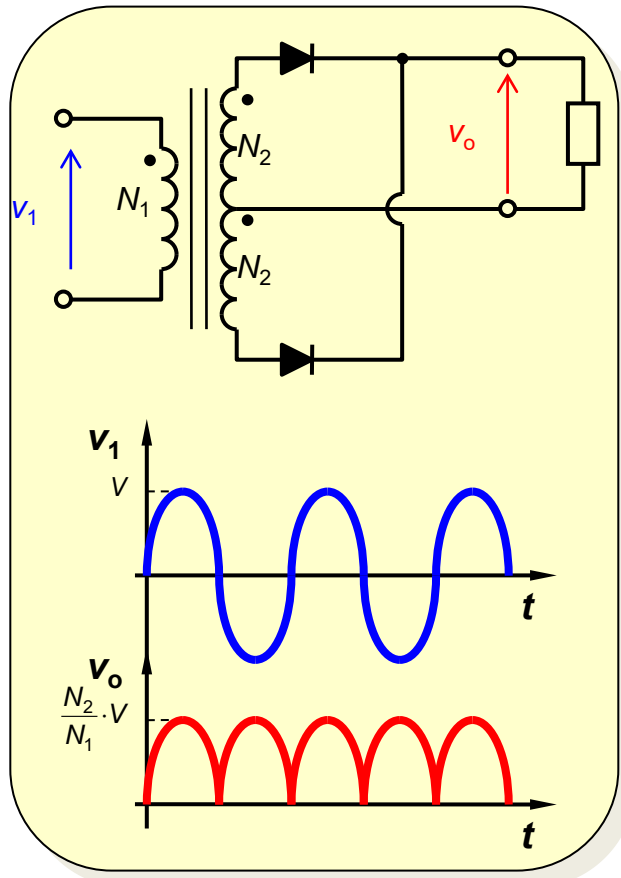
### Full-wave Rectifier: with tapped secondary



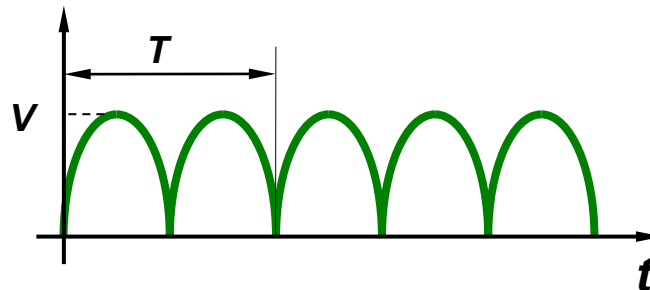- During each hemicycle only one diode conducts.
- Each diode supports an inverse voltage of the double of the maximum voltage value of each winding of the secondary.




$$V_{cc} = \frac{2V}{\pi}$$


## 2. Initial stages. Rectifier

- **The selection of the diodes depends on the voltages and currents required in the specific application.**
  - Average forward current,  $I_{F(AV)}$
  - Peak working reverse voltage,  $V_{RWM}$
  - Repetitive forward peak current,  $I_{FRM}$
  
- **“General purpose” diodes are commonly used.**
  - Designed to work at low frequencies in rectification applications (< 400 Hz).
  - They can support currents of 1 to 25 A, with reverse voltages of 50 to 1000 V.
  - Rectifying bridges with 4 diodes are also available as integrated circuits.

## 2. Initial stages. Filter

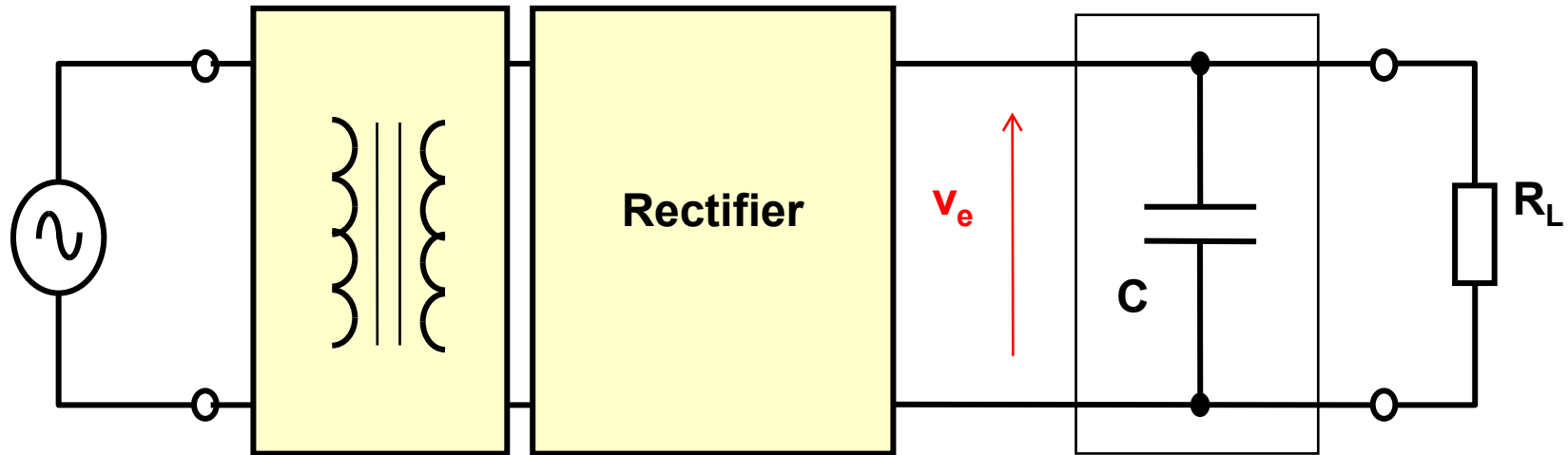


# 2. Initial stages. Filter

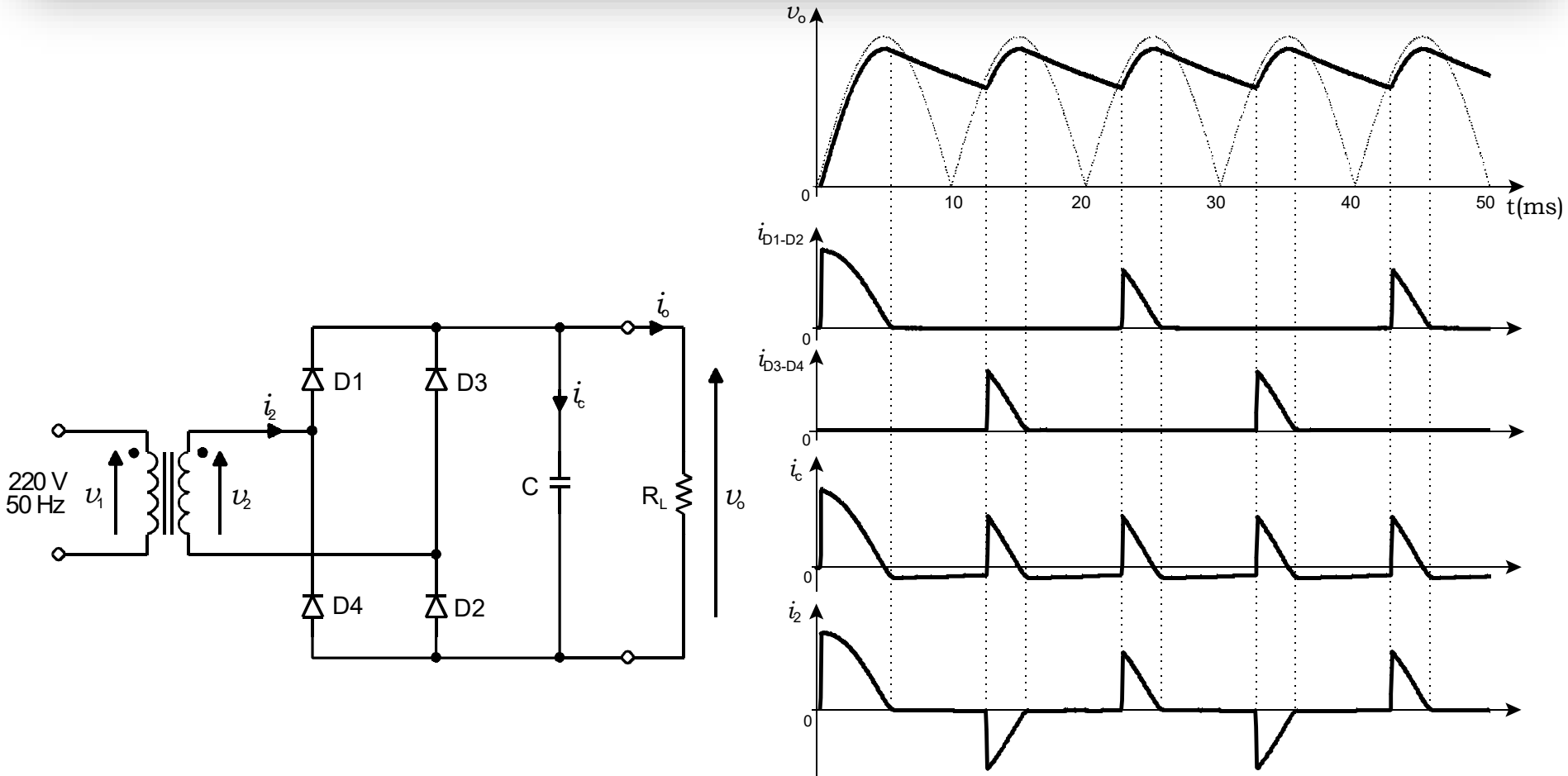

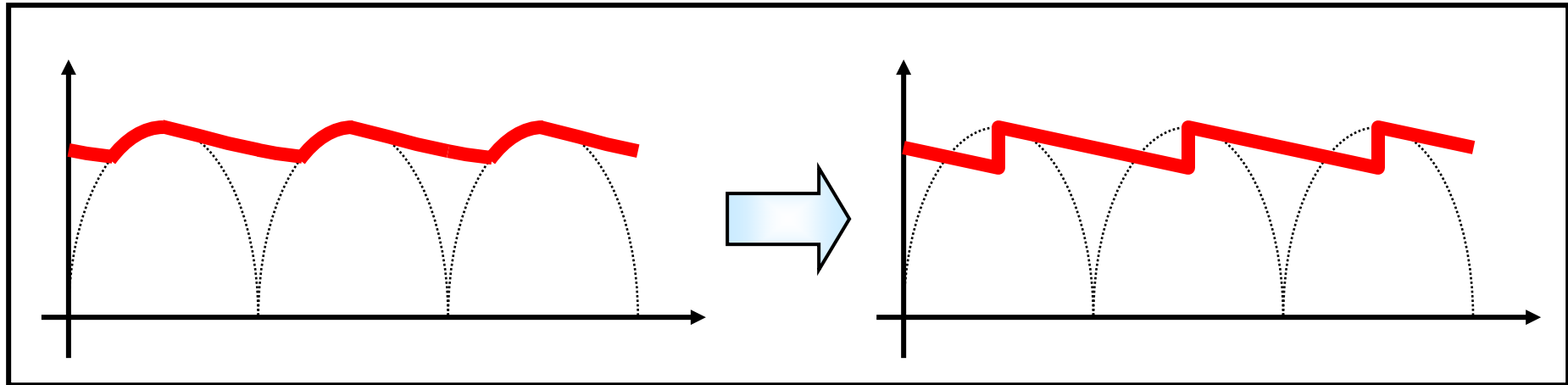
## 2. Initial stages. Filter

- **Output voltage: exponential and sinusoidal**
  - The detailed analysis is complex
- **Aproximation to a triangular waveform → simplification**
  - Considers a lineal discharge of the capacitor ( $RL \cdot C \gg T/2$ )
  - Supposes an instantaneous charge of C when the diodes conduct



## 2. Initial stages. Filter

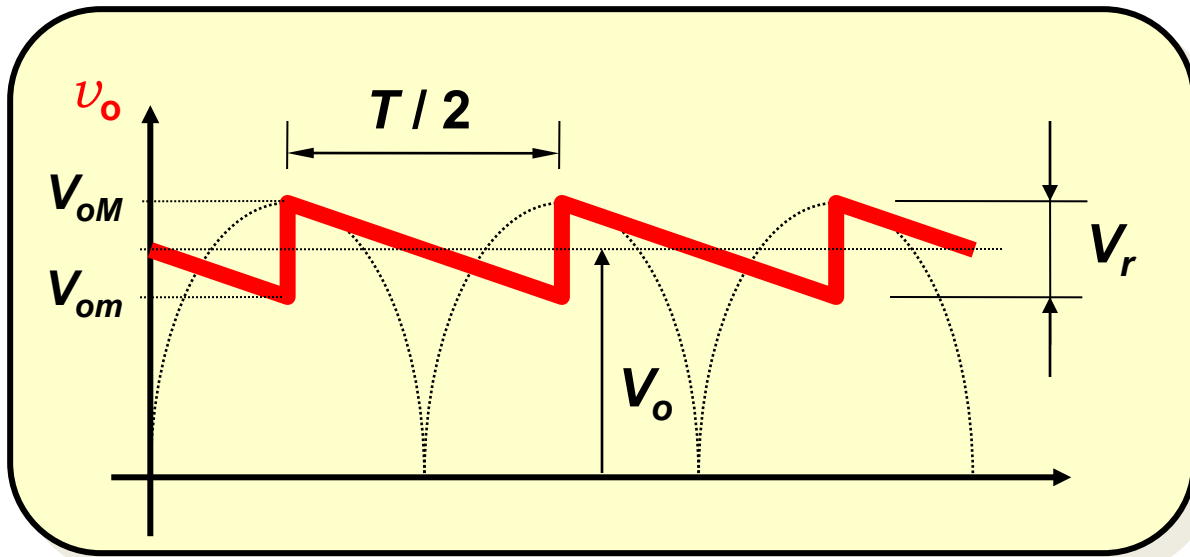

➤ Assumes discharge of C at constant current.

$$i_C = i_{load} = I_o$$


$$I_o \approx \frac{V_{o(cc)}}{R_L} = \frac{V_o}{R_L}$$

➤ The value of  $V_r$  is usually known

- Limited by the specifications
- Allows the calculation of C
- Tolerances must be considered ( $\pm 20\%$ )


$$V_r = \frac{V_o}{2fR_LC} = \frac{I_o}{2fC}$$

# 2. Initial stages. Filter

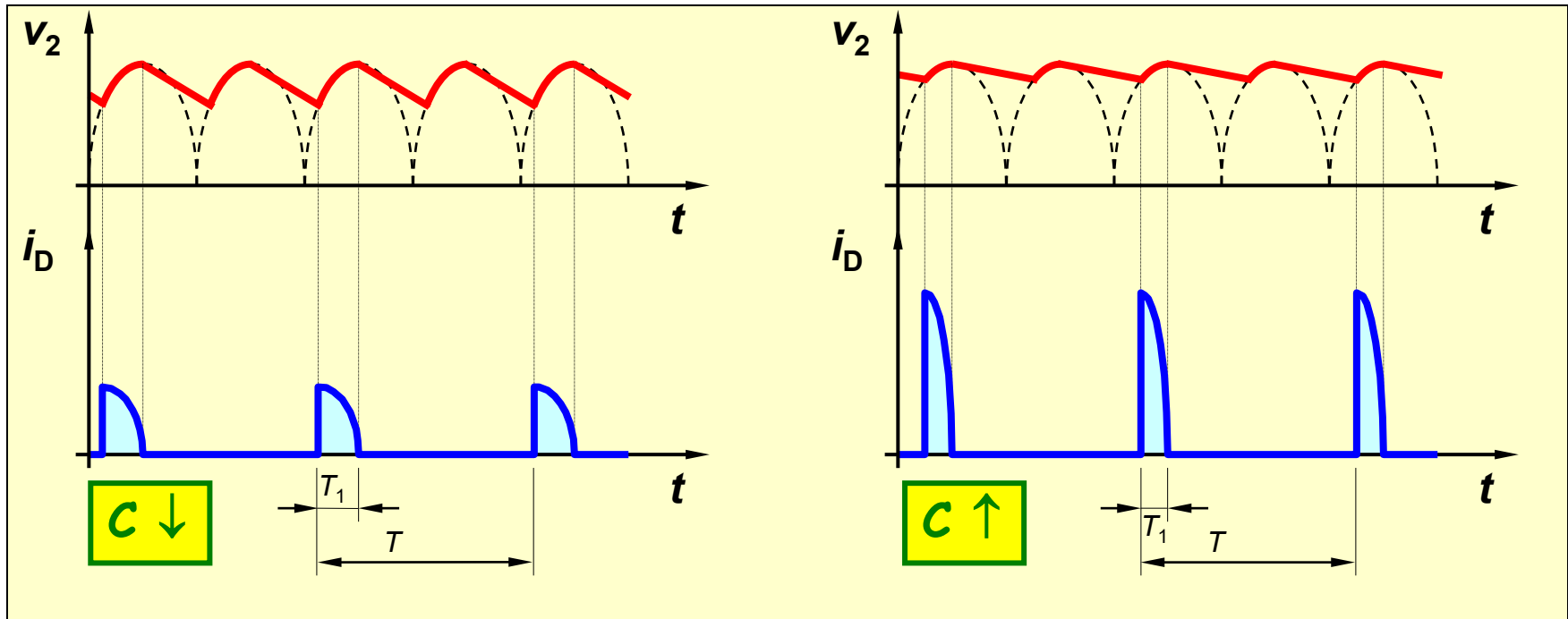


$$I_{D(\text{peak})} \cong \frac{T}{T_1} I_{dc}$$

# 3. Classification

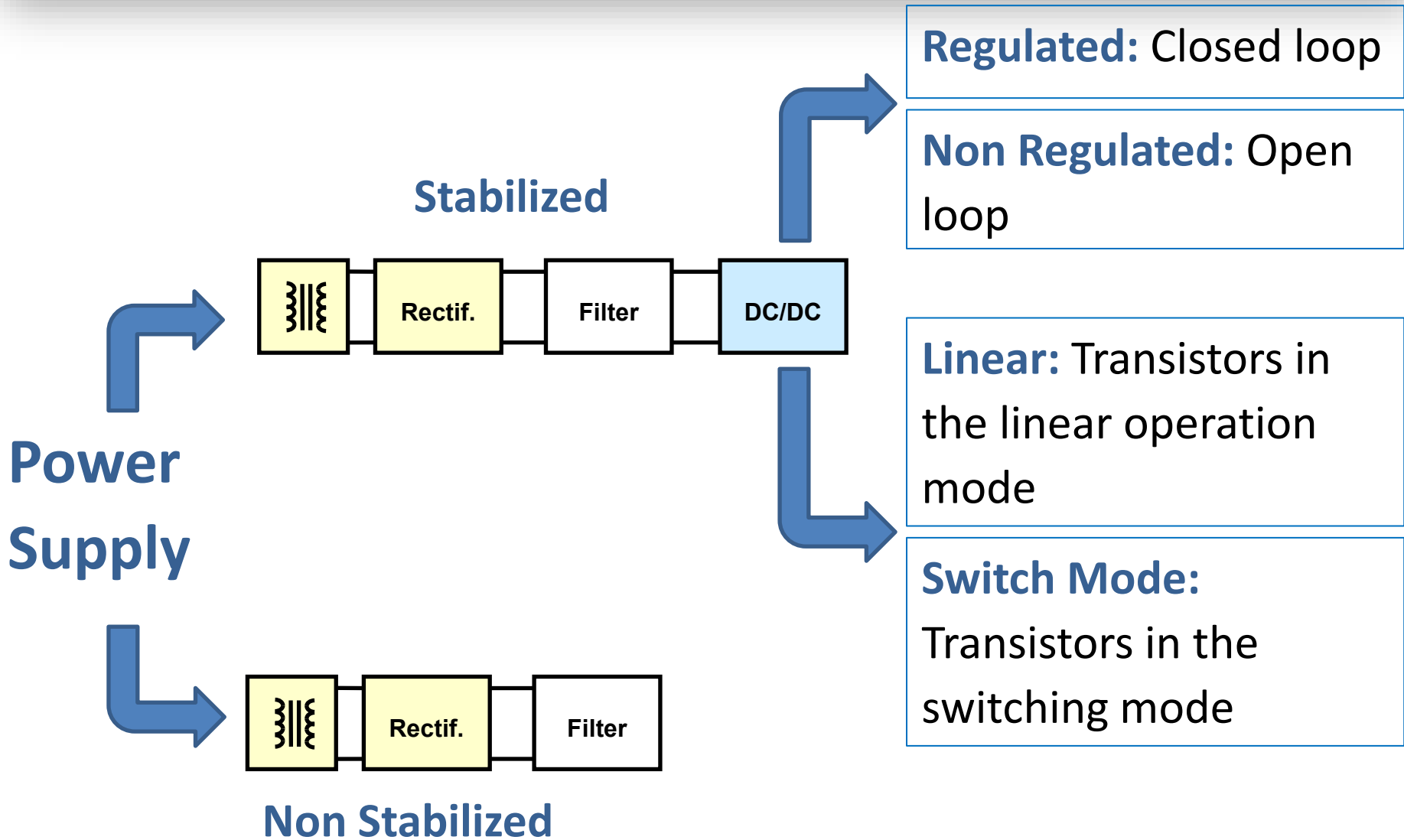




# 4. Stabilized Power Supplies

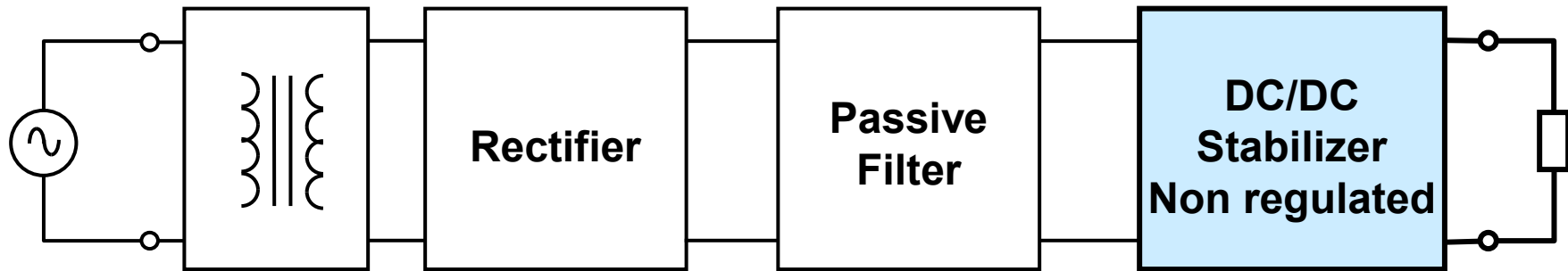


# 4. Stabilized Power Supplies

Non  
Regulated  
Supply  
Source

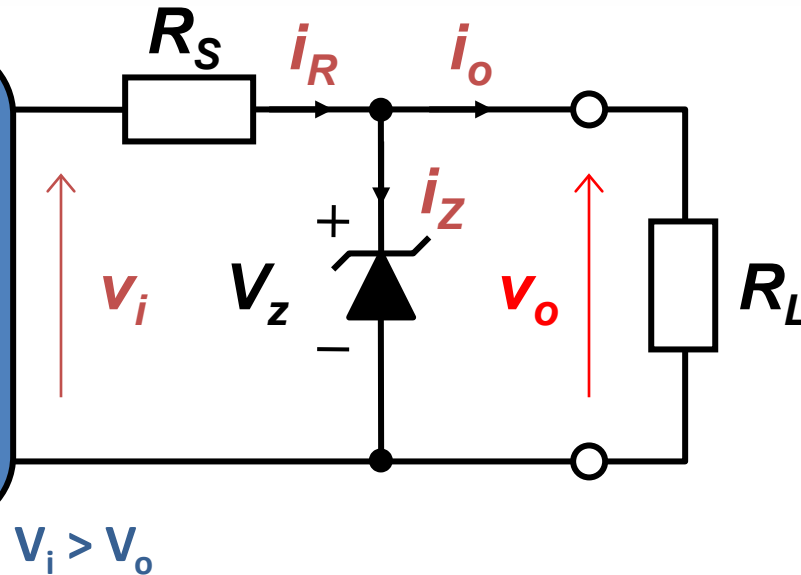

$$v_o = V_z$$

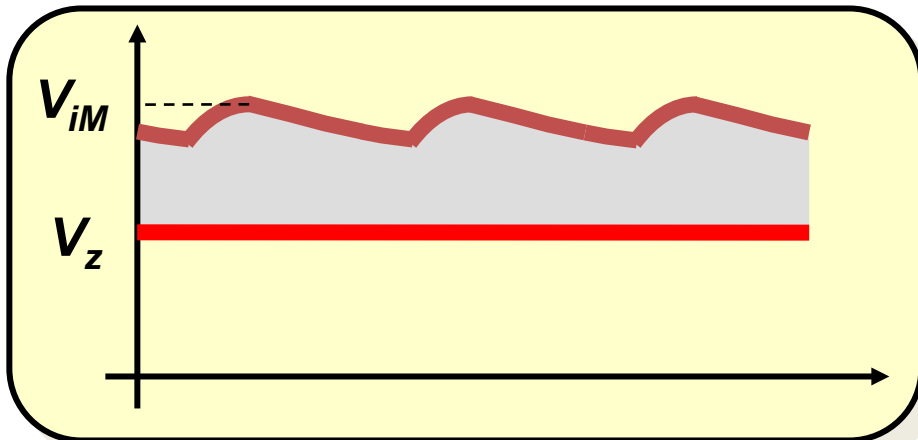


The difference of both voltages is supported by  $R_S$

- $v_i$  should not be much higher than  $v_o$ .  $V_o = V_i R_L / (R_L + R_S) > V_z$
- Election of  $N_2 : N_1$ .

# 4. Stabilized Power Supplies
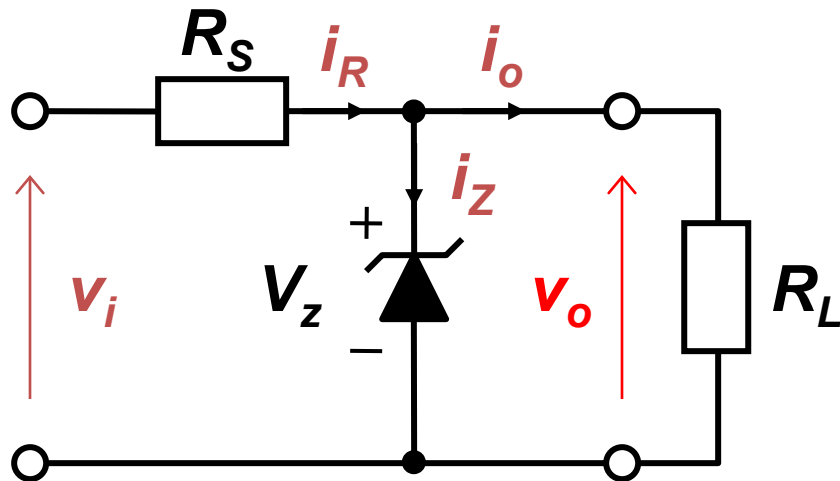
## ➤ Operation Limits

- $I_{z(min)} \leq i_z \leq I_{z(max)}$
- Current in  $R_S$ :  $I_{R(min)} = I_{o(max)} + I_{z(min)}$



$$\frac{V_{i(min)} - V_z}{I_{o(max)} + I_{z(min)}} \geq R_S \geq \frac{V_{i(max)} - V_z}{I_{o(min)} + I_{z(max)}}$$

## $R_S$ should be big enough:

- Less warming up of the zener
- $V_o$  is less affected by fluctuations in  $V_i$

## ➤ Main drawback:

- If the circuit is designed for high  $I_o$ , the zener diode should support such currents → power zener diode


# 5. Regulated Power Supplies

## ➤ Limitations of stabilizing circuits:

- The accuracy of the output voltage depends on the features of the used electronic devices.
- Lack of control of the output voltage.
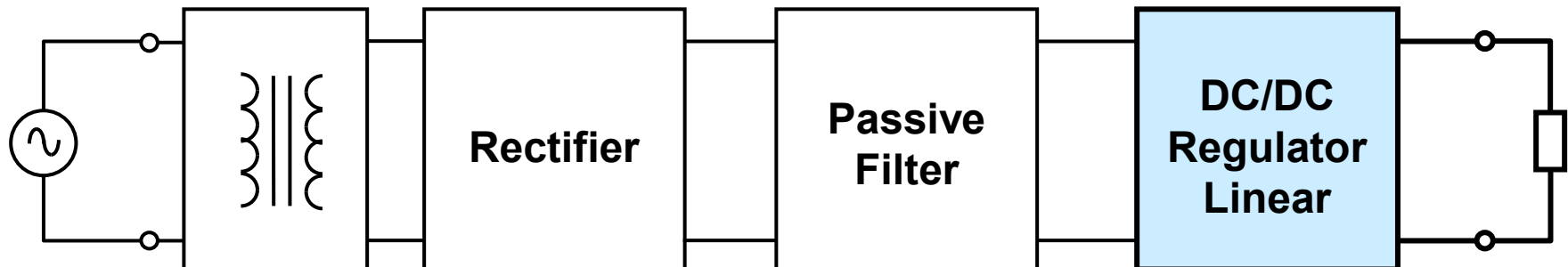
## ➤ Linear Regulator → maintains constant the output voltage

- System with negative feedback to maintain constant the output voltage when the load or the input voltage variates.




# 5. Regulated Power Supplies
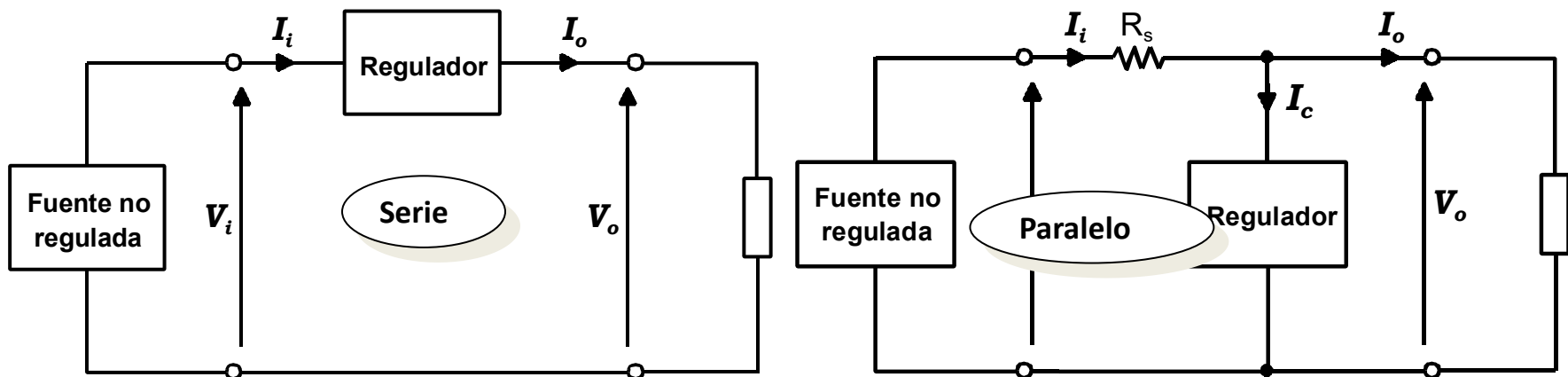
## ➤ Two kinds of regulators: series and shunt


Variations in the output voltage provoked by changes in the non-regulated voltage and in the output current are compensated by variations in:

- The voltage drop of an element situated in series with the load ➔ **Series Regulator** (the most common)
- The current of an element situated in parallel with the load ➔ **Shunt Regulator**



# 5. Regulated Power Supplies. Series.

## Blocks diagram of a serie regulator:

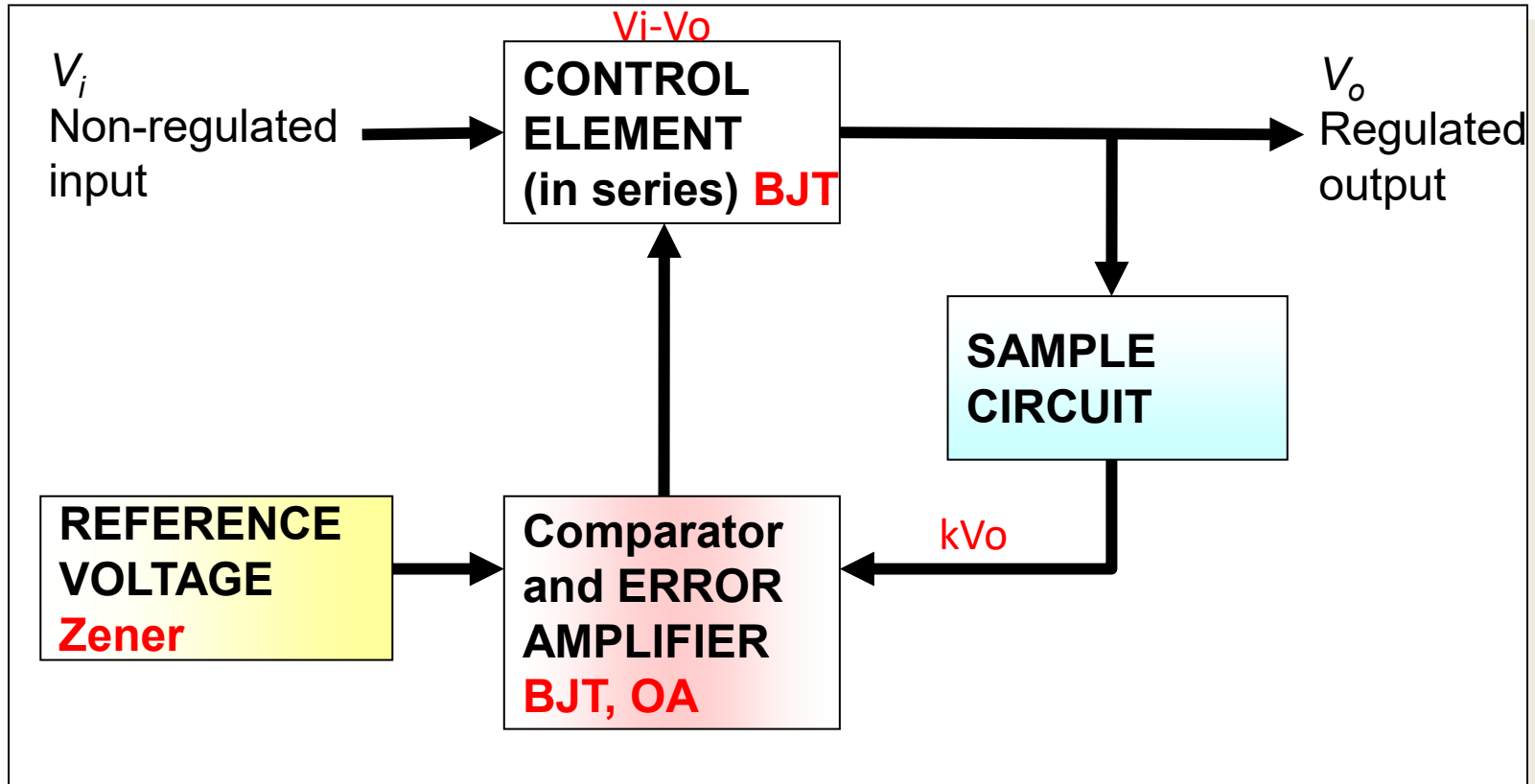

Feedback:  $\uparrow V_o \rightarrow \text{control} \uparrow (V_i - V_o) \rightarrow \downarrow V_o$

# 5. Regulated Power Supplies. Series.

## ➤ Reference circuit:

- Provides a stable reference voltage.
- Usually based on a zener diode.
- Simplest solution → zener diode + polarizing resistor.

## ➤ Sample circuit:

- Provides a signal proportional to the output signal.
- Usually composed by a resistor divider connected to the output.


## ➤ Error amplifier:

- Compares the sampled voltage with the reference voltage and generates an error signal proportional to the difference.

## ➤ Control element:

- Receives the error signal and corrects the variations of the output voltage.
- Is usually composed by a bipolar transistor (NPN usually) connected in series between the input and output of the regulator.

# 5. Regulated Power Supplies. Series.

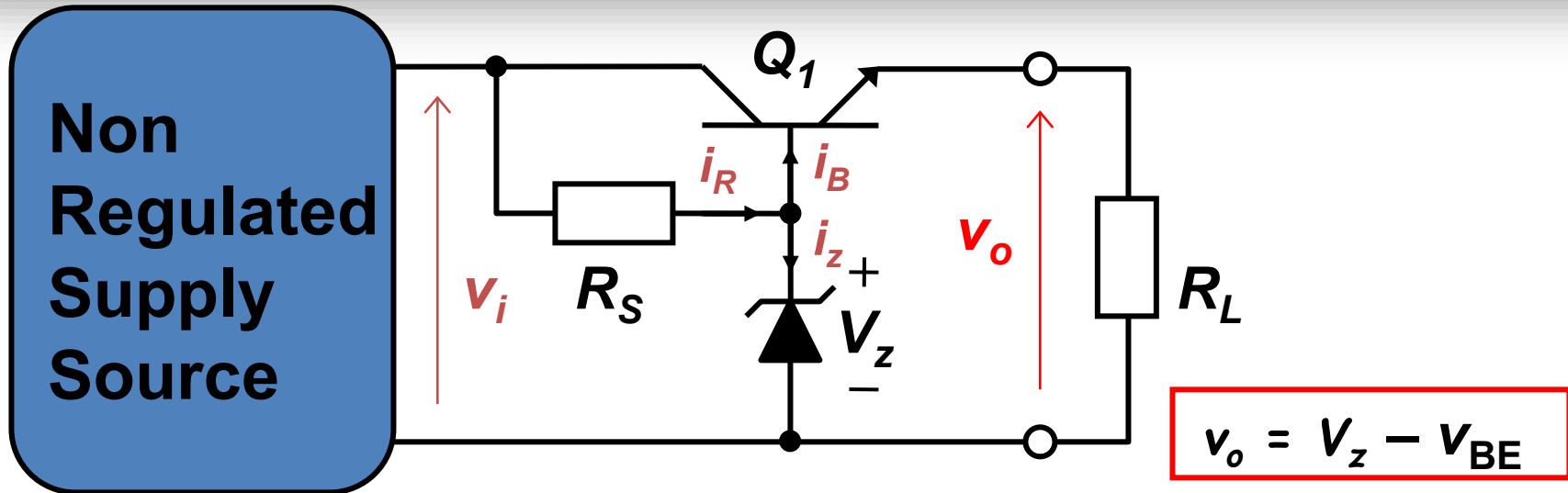

- The transistor dissipates the power generated by  $v_i - v_o$ .

- Design of  $R_S \rightarrow R_{S(\max)} = \frac{V_{i(\min)} - V_Z}{I_{z(\min)} + \frac{I_{o(\max)}}{\beta + 1}}$

- The zener diode does not need to support elevated currents.

Feedback:  $\uparrow v_o \rightarrow \downarrow V_{BE} \rightarrow \downarrow I_E = (1 + \beta) I_{SS} e^{V_{BE}/V_T} \rightarrow \downarrow I_o \rightarrow \downarrow v_o$




**P50.** En el circuito de la figura calcular:

a) Tensión de salida que fija el regulador en la carga  $R_L$

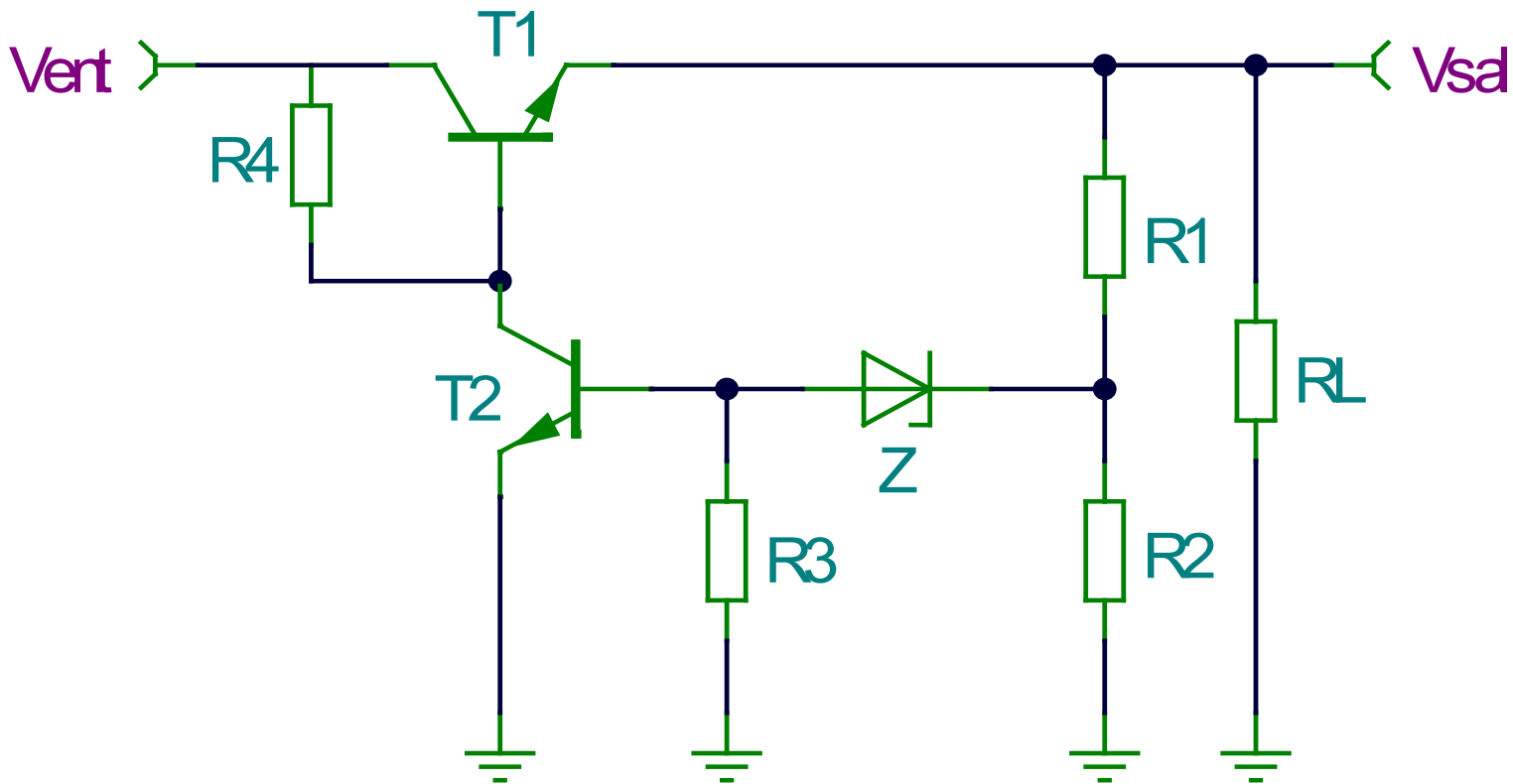b) Tensión y corriente en cada una de las resistencias del circuito.


Datos:  $R_1 = 3.3 \text{ k}\Omega$ ,  $R_2 = 2.2 \text{ k}\Omega$ ,  $R_3 = 5 \text{ k}\Omega$ ,  $R_4 = 10 \text{ k}\Omega$ ,  $R_L = 2 \text{ k}\Omega$

$V_{ent} = 40 \text{ V}$ ,  $V_Z = 10 \text{ V}$ . Para T1 y T2:  $V_{BE} = 0.7 \text{ V}$ ,  $\beta = 100$



# 5. Regulated Power Supplies. Series.

## OA series regulator:

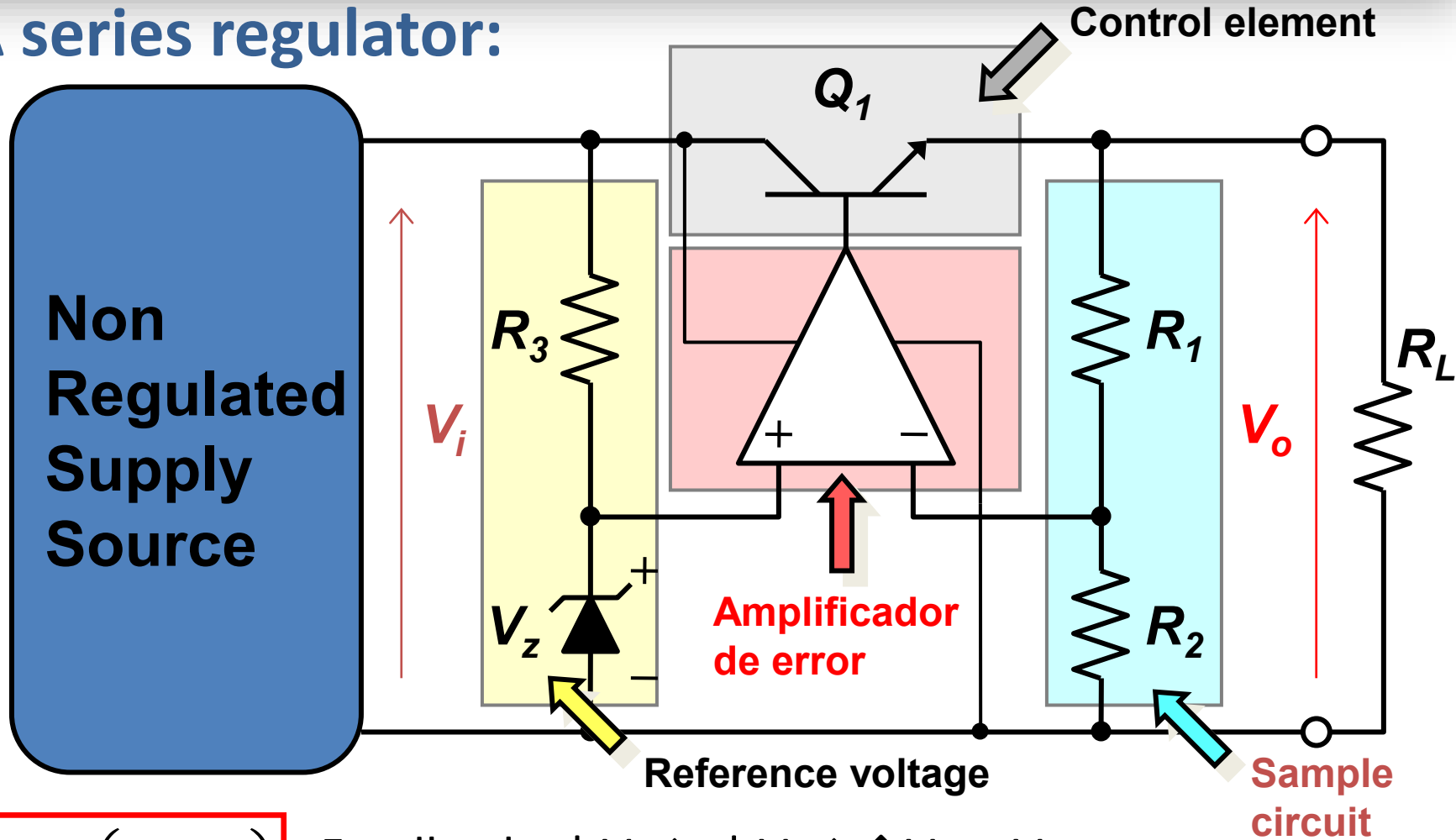


$$V_o = V_R \left( 1 + \frac{R_1}{R_2} \right)$$

Feedback:  $\downarrow V_o \rightarrow \downarrow V_- \rightarrow \uparrow V_{AO} = V_B$   
 $\rightarrow \uparrow I_B \rightarrow \uparrow I_O \rightarrow \uparrow V_o$

# 5. Regulated Power Supplies. Series.

## OA series regulator:

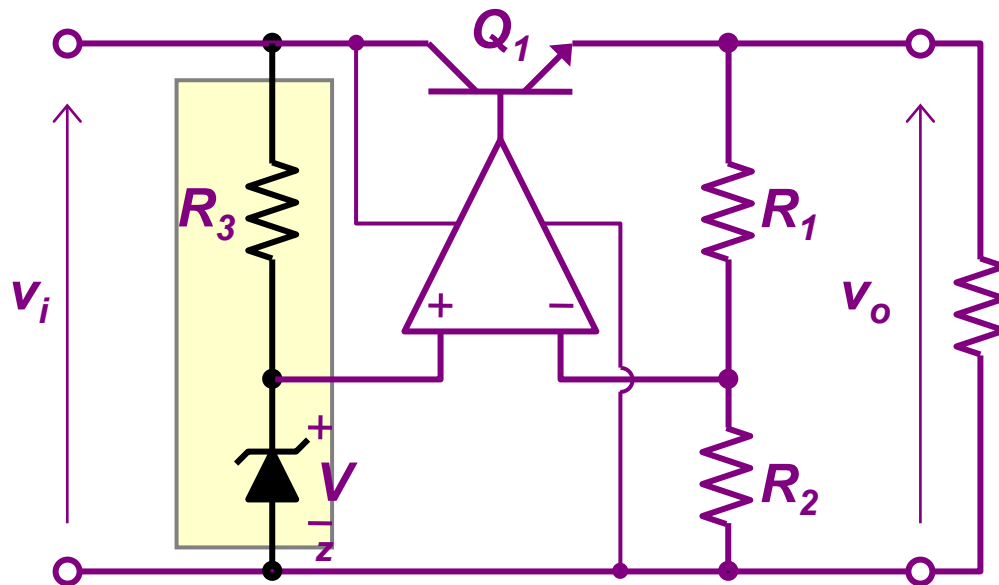


## Reference Voltage:

- Simple circuit.
- Select  $R_3$  high enough to reduce the effect of the ripple of  $v_i$ .
- Also LEDs, rectifying diodes, IC reference circuits (LM336).

# 5. Regulated Power Supplies. Series.

## OA series regulator:

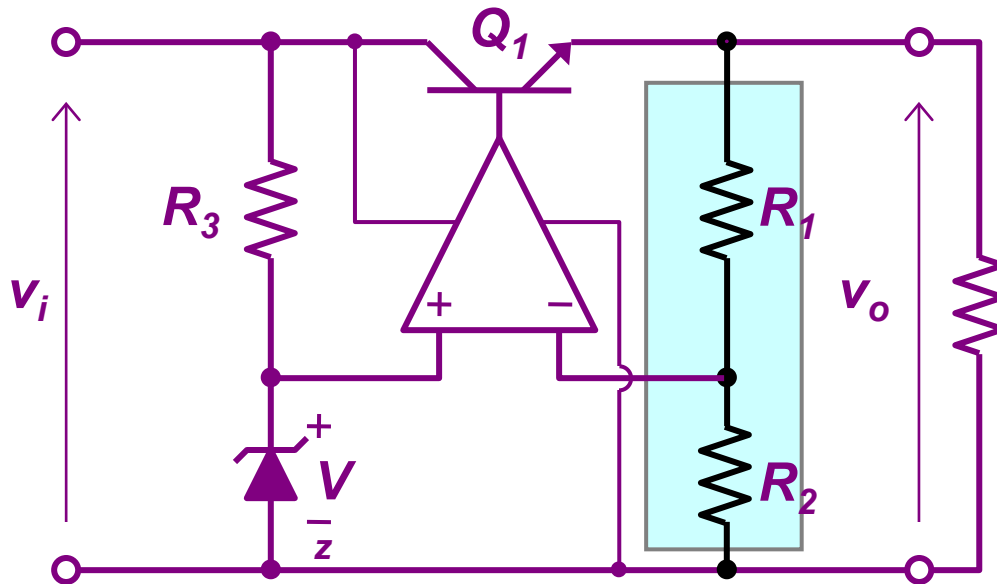

## Sample circuit


- Very simple circuit.
- The supported current must be negligible versus the load current.



**$R_1$  and  $R_2$  high values compared to the load.**

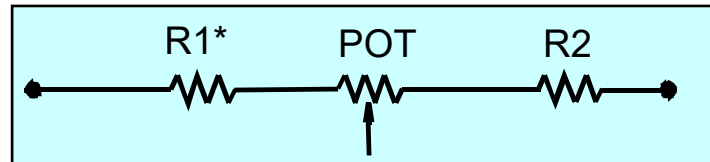
## To allow $V_o$ adjustment:

A potentiometer should be used in the voltage divider.



# 5. Regulated Power Supplies. Series.
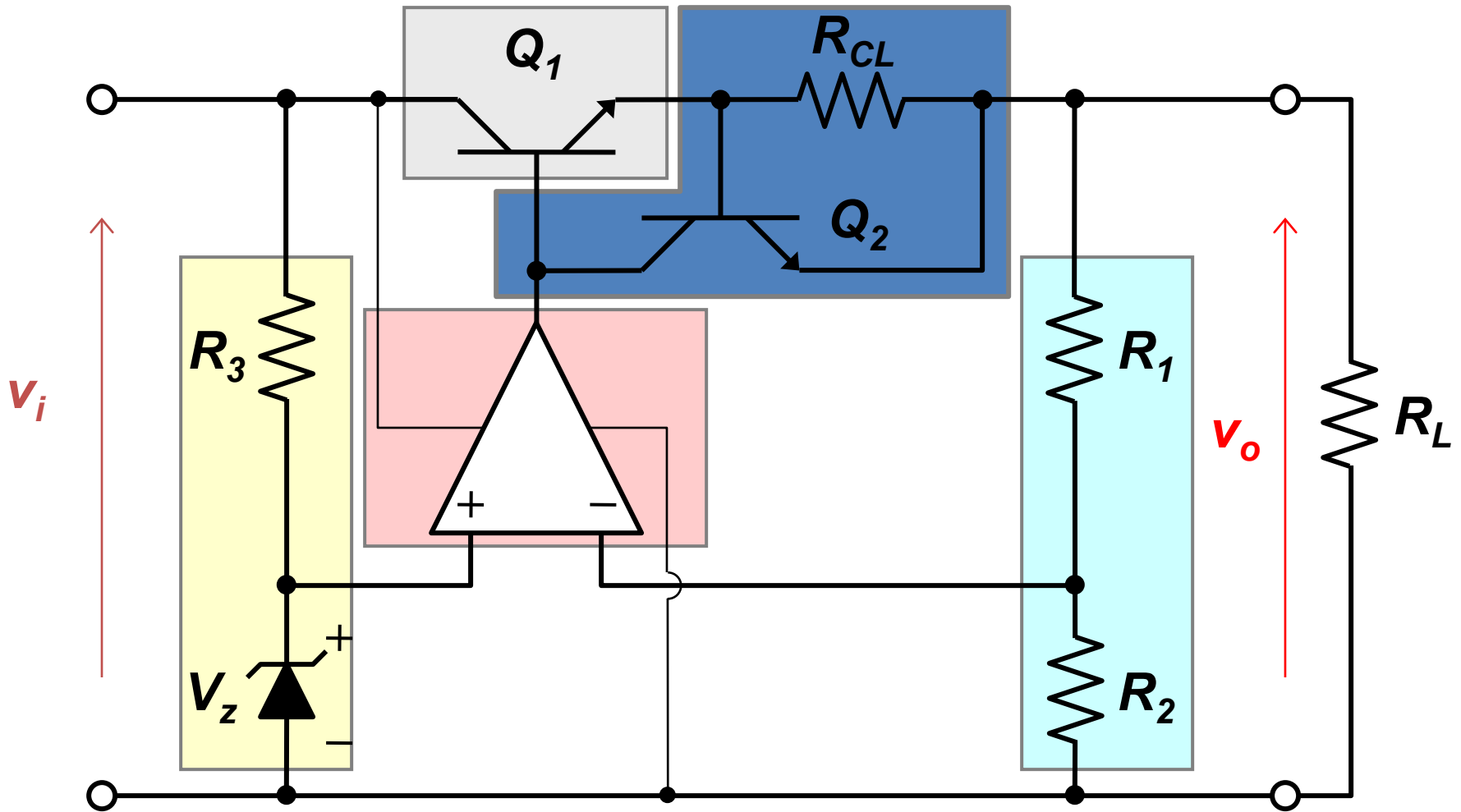
## OA series regulator: current limitation





# 5. Regulated Power Supplies. Series.

## OA series regulator:
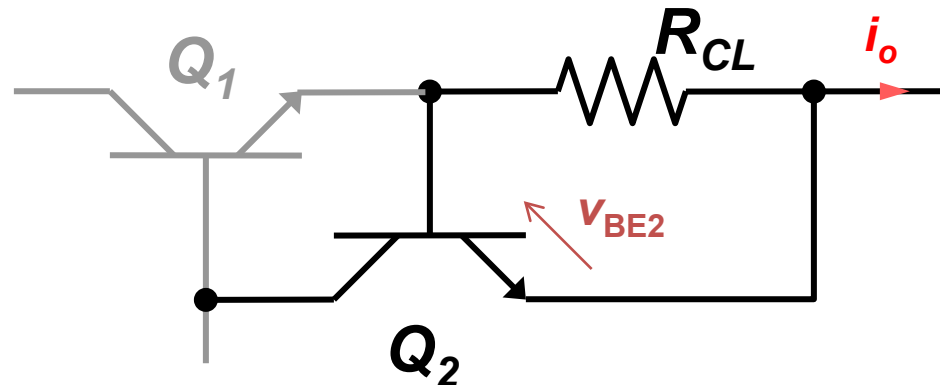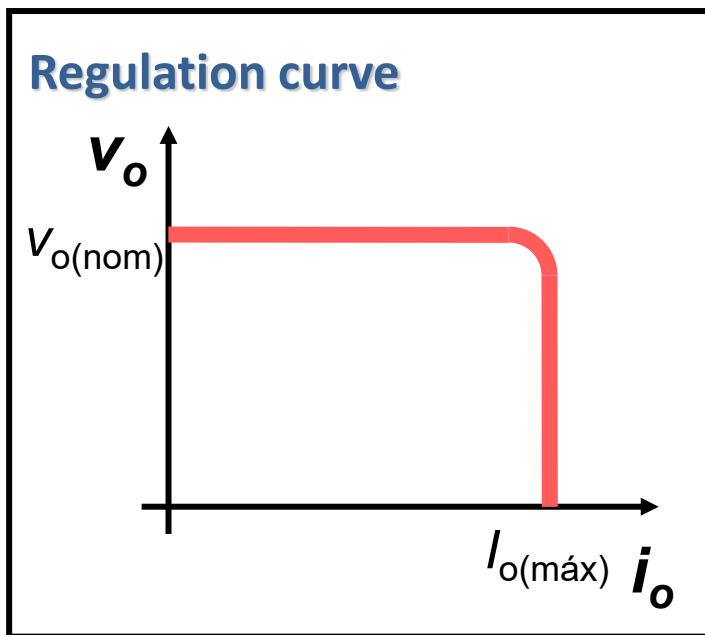
### ➤ Limitation at constant current.

- If  $i_o < I_{o(max)}$ , then  $v_o = v_{o(nom)}$ .
- If  $i_o > I_{o(max)}$ ,  $v_o$  decreases  $\rightarrow 0 \leq v_o \leq v_{o(nom)}$ .

$$I_{o(max)} = I_{SC} = \frac{V_{BE2(ON)}}{R_{CL}}$$



If  $Q_2$  conducts, it “steals” base current to  $Q_1$ .

- $i_o$  is then limited.
- The value of  $I_{o(max)}$  is fixed by  $R_{CL}$ .

In shortcircuit:  $P_{Q1} \approx v_i \cdot I_{o(max)}$

**P52.** En el circuito de la figura calcular:

a) Tensión de salida que fija el regulador

b) Corriente en la resistencia R3


c) Corriente mínima y máxima en la resistencia R4.

d) Calcular la resistencia limitadora Rlim

Podemos desprejir las corrientes por R1 y R2 para facilitar los cálculos.


Datos:  $R1 = 100\text{ k}\Omega$ ,  $R2 = 50\text{ k}\Omega$ ,  $R3 = 5\text{ k}\Omega$ ,  $R4 = 50\text{ }\Omega$ ,  $POT = 0.55\text{ k}\Omega / 3\text{ W}$

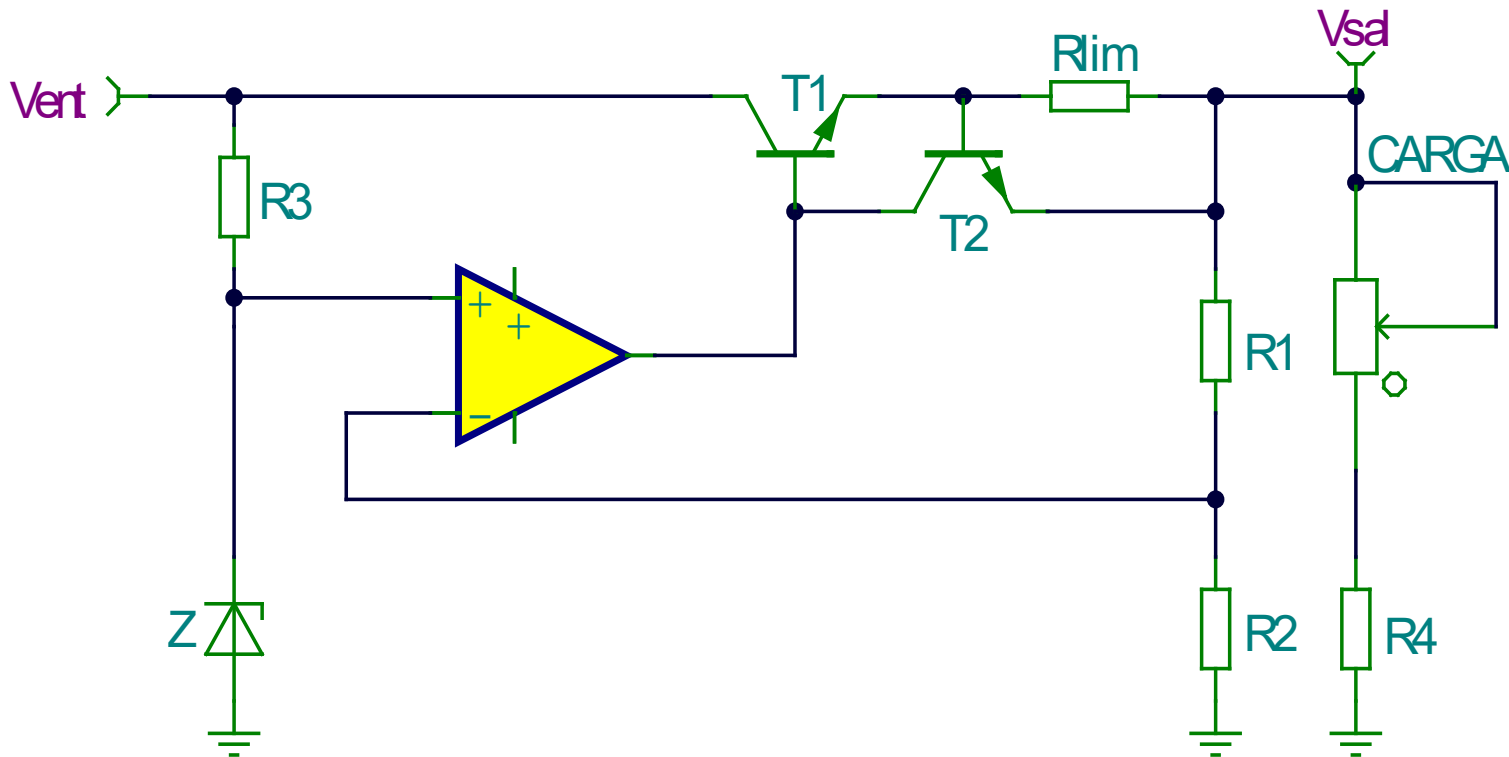$V_{ent} = 35\text{ V}$ ,  $V_Z = 10\text{ V}$ ,  $I_{Zmin} = 1\text{ mA}$ ,  $P_{Zmax} = 0.5\text{ W}$ ,  $V_{BE} = 0.6\text{ V}$



# 5. Regulated Power Supplies. Shunt.

## Shunt regulator:

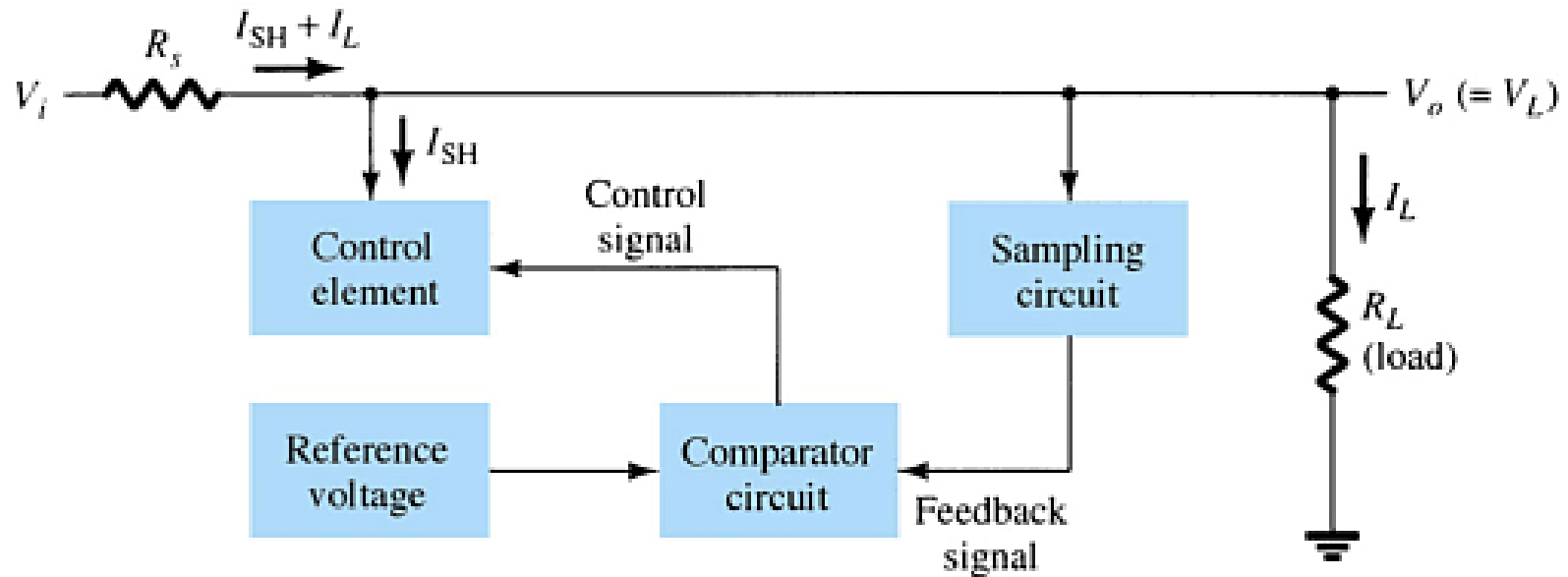


Feedback:  $\uparrow V_o \rightarrow \text{control} \uparrow I_{SH} \rightarrow \downarrow I_L \rightarrow \downarrow V_o$



# 5. Regulated Power Supplies. Shunt.

## Shunt regulator:

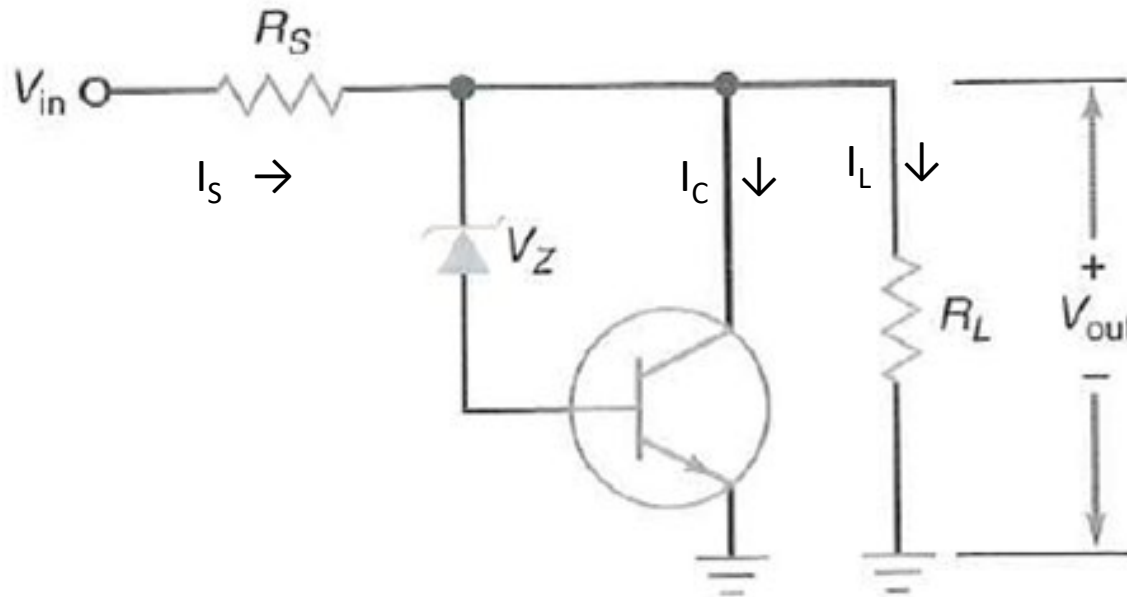

$$V_{out} = V_z + V_{BE}$$

$$I_S = \frac{(V_{in} - V_{out})}{R_S}$$


$$I_L = \frac{V_{out}}{R_L}$$

$$I_C \cong I_S - I_L$$

Feedback:  $\downarrow R_L \rightarrow \downarrow V_o \rightarrow \downarrow V_{BE} \rightarrow \downarrow I_Z \rightarrow \downarrow I_C \rightarrow \uparrow I_L \rightarrow \uparrow V_o$   
 $V_o$  remains constant ( $R_L$  fluctuations compensated by  $I_L$  fluctuations)

# 5. Regulated Power Supplies. Shunt.

## OA shunt regulator with OA:

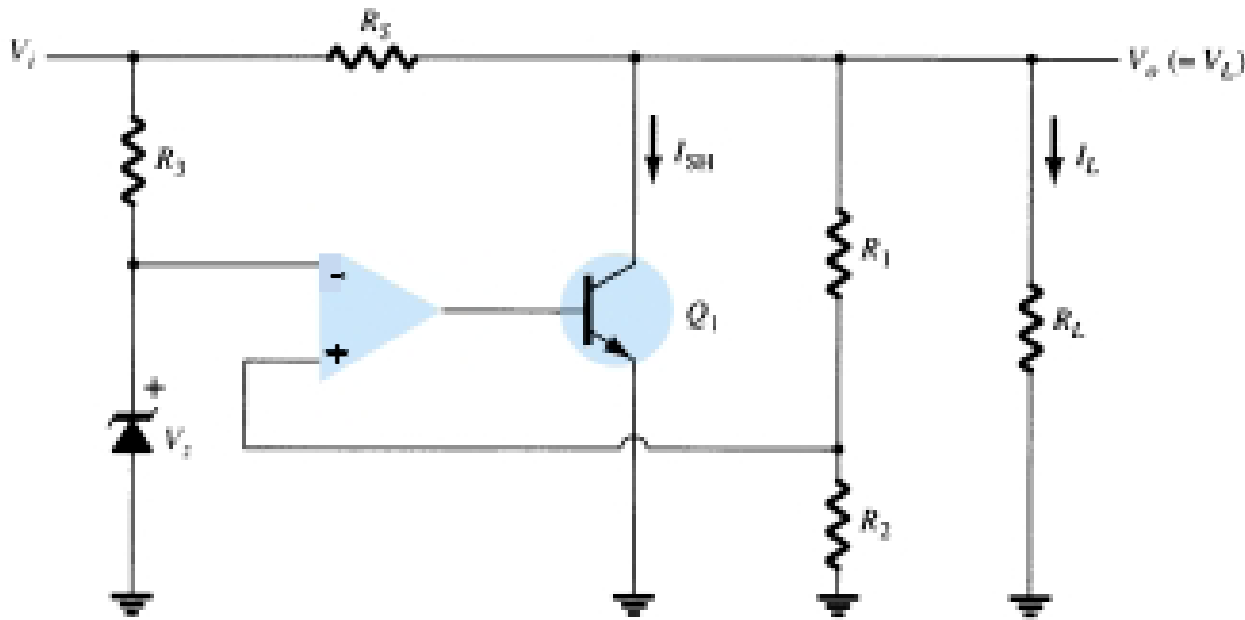

$$V_{out} = \frac{R_1 + R_2}{R_1} \cdot V_z$$


$$I_L = \frac{V_{out}}{R_L}$$

$$P_D \approx (V_{in} - V_{out}) \cdot I_L$$

Feedback:  $\downarrow V_o \rightarrow \downarrow V_+ \rightarrow \downarrow V_{AO} = V_B \rightarrow \downarrow I_{SH} \rightarrow \uparrow I_L \rightarrow \uparrow V_o$

# 5. Regulated Power Supplies. Shunt.

## Shunt regulated power supply with OA

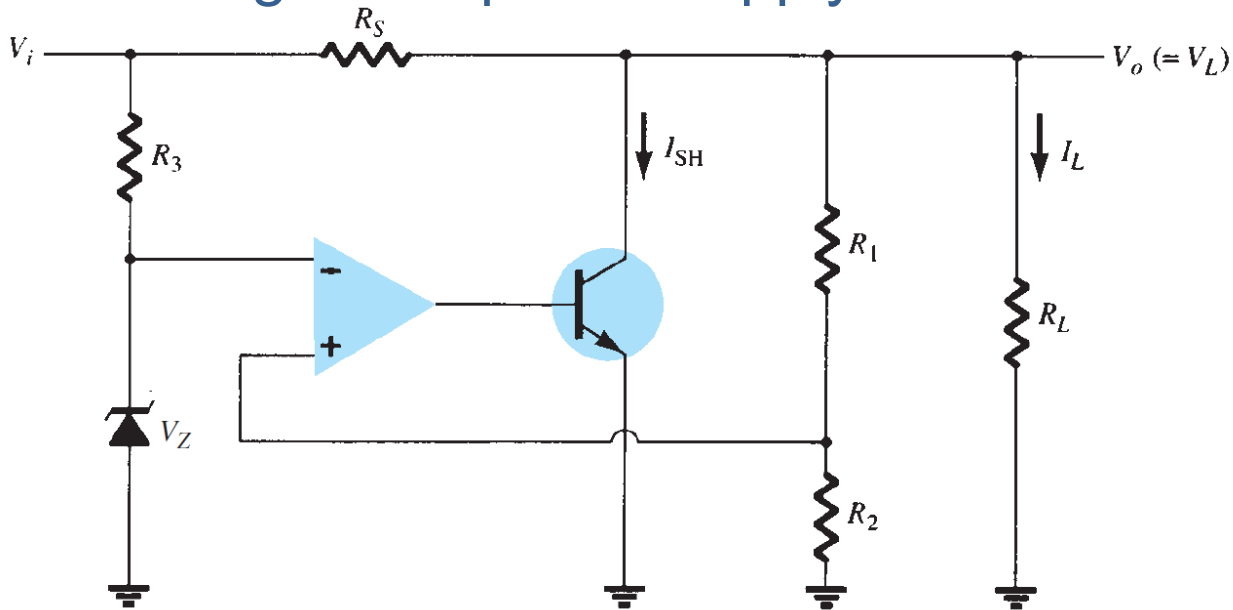

**Exercise.** OA (741C,  $\pm 15$  V,  $I_{o-max}=25$  mA),  $R_s=1.5$   $\Omega$ ,  $V_i=20-22$  V,  $I_L=0.8-1.2$  A,  $V_z=5$  V, BJT ( $\beta=100-400$ ,  $V_{be-on}=0.65$  V)  
 1) Design  $R_1$  and  $R_2$  for  $V_o=18$  V. Calculate: 2) Range of  $I_{SH}$  and check the non-saturation of the OA. 3) Maximum power in  $R_s$  and BJT.

# 6. Integrated Power Supplies

- **They appeared because of the need of regulators in the power supplies.**
- First generation → components of general application.
  - The big demand of specific voltage supplies (5V for instance) led to the manufacturing of fixed voltage regulators with only 3 terminals.
  - Low cost, easy to use.
  - Later voltage regulators with 3 terminals but with adjustable voltage were developed.
    - Low cost + easy to use + versatility.

# 6. Integrated Power Supplies

## ➤ Classification:


- Regulators of multiple terminals.
- Regulators of 3 terminals:
  - fixed voltage:
    - positive
    - negative
  - adjustable voltage:
    - positive
    - negative

# 6. Integrated Power Supplies


## Regulators of multiple terminals

- Based on the linear basic regulator.
- Several parts of the circuit are independent and can be connected by the user.
- Most representative examples:

- $\mu$ A723 (14 terminales)

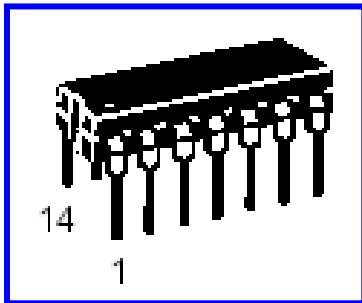

- L200 (5 terminales).

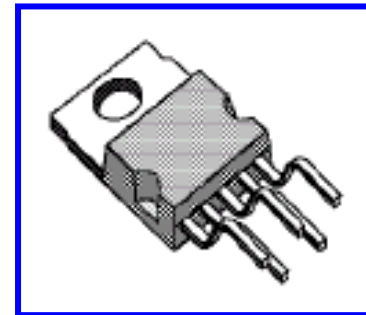


# 6. Integrated Power Supplies

## Regulators of multiple terminals: L200



<40 V

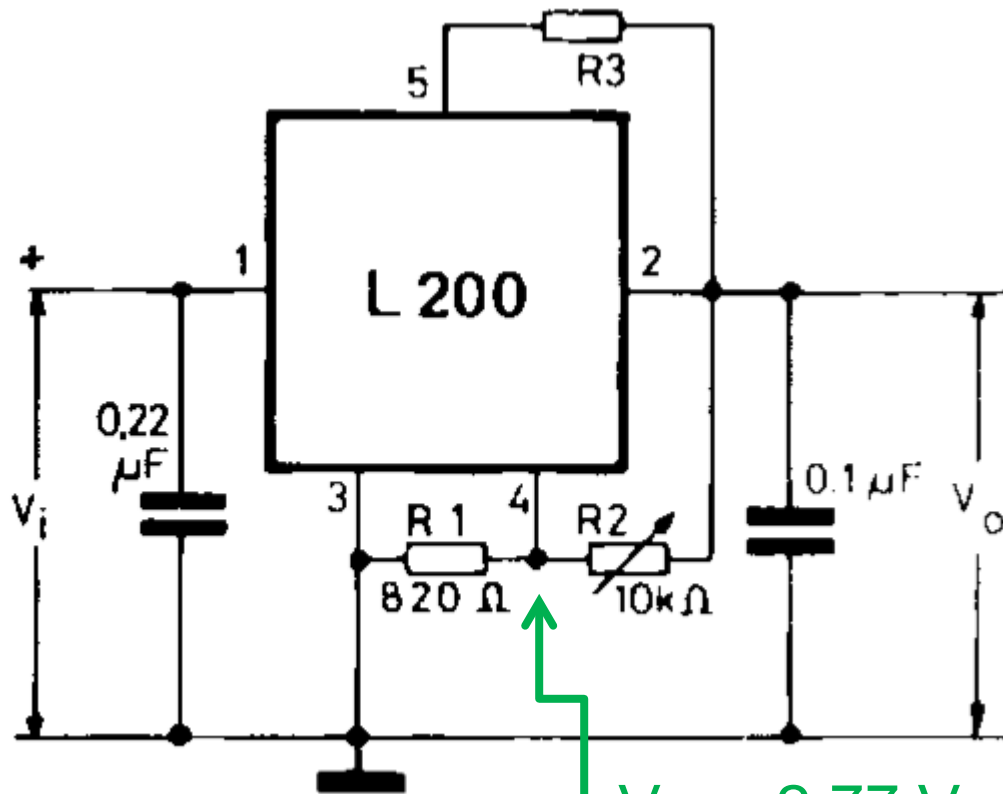


$$V_O = V_{\text{ref}} \cdot (1 + R_2/R_1)$$

$$V_{\text{ref}} = 2.77 \text{ V} \quad (V_i = 20 \text{ V})$$

# 6. Integrated Power Supplies

## Regulators of multiple terminals

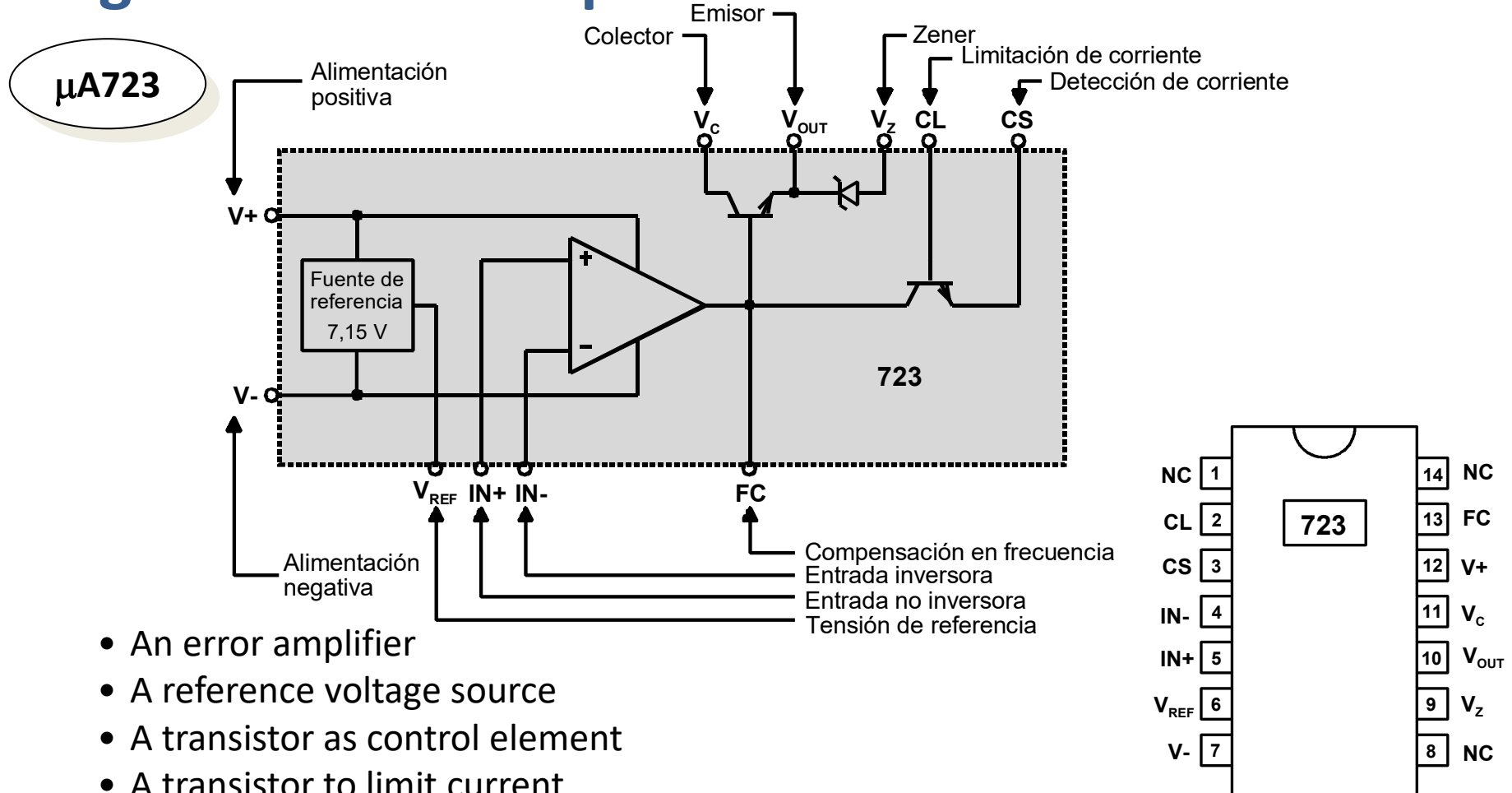


- An error amplifier
- A reference voltage source
- A transistor as control element
- A transistor to limit current
- A zener diode for specific applications
- A terminal for frequency compensation



# 6. Integrated Power Supplies

## Regulators of multiple terminals

$\mu$ A723

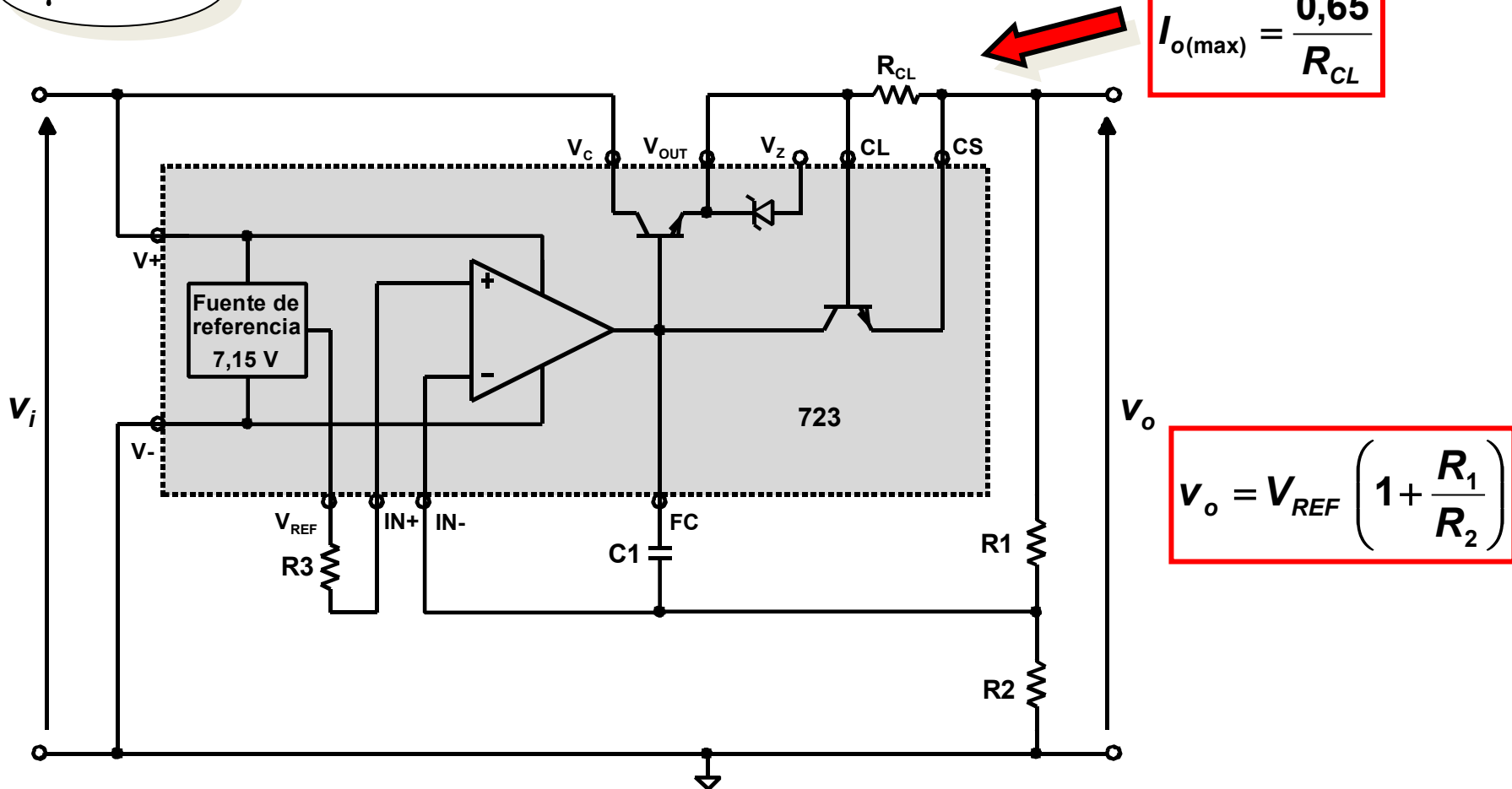

$$I_{o(max)} = \frac{0,65}{R_{CL}}$$





$$V_o = V_{REF} \left( 1 + \frac{R_1}{R_2} \right)$$

Output voltage higher than the reference voltage (7 to 37 V)

# 6. Integrated Power Supplies
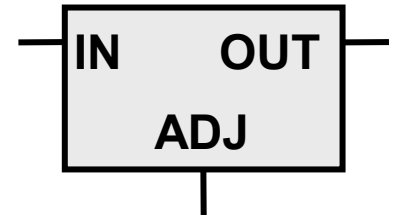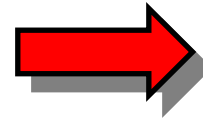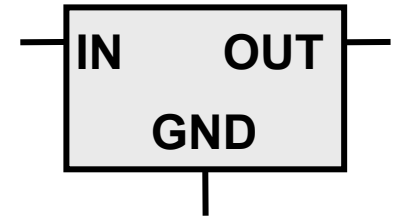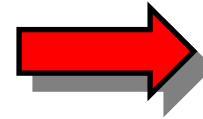
## Regulators of 3 terminals

- Regulated output.
- Simple use and low cost.
- Two types:
  - **Fixed regulators:** provide a fixed voltage (positive or negative).
  - **Adjustable regulators:** the output voltage (positive or negative) can be adjusted using external components.



# 6. Integrated Power Supplies

## Regulators of 3 terminals

- Regulators 78XX provide positive voltages, whereas 79XX provide negative voltages.
- The last 2 digits XX, indicate the output regulated voltage.

Type	$I_{o(max)}$ (A)
78LXX-79LXX	0,1
78MXX-79MXX	0,5
78XX-79XX	1
78TXX-79TXX	3

Tipo	$V_o$ (V)	$V_{i(min)}$ (V)	$V_{i(max)}$ (V)
7805	5	7	35
7806	6	8	35
7808	8	10	35
7809	9	11	35
7810	10	12	35
7812	12	14	35
7815	15	17	35
7818	18	20	35
7824	24	26	40
79XX	Same values but negative		


- Datasheets:
  - LM78XX  $\Rightarrow$  National Semiconductor, Fairchild.
  - UA78XX  $\Rightarrow$  Texas Instruments
  - MC78XX  $\Rightarrow$  Motorola, ON Semiconductors,...

# 6. Integrated Power Supplies

## Regulators of 3 terminals
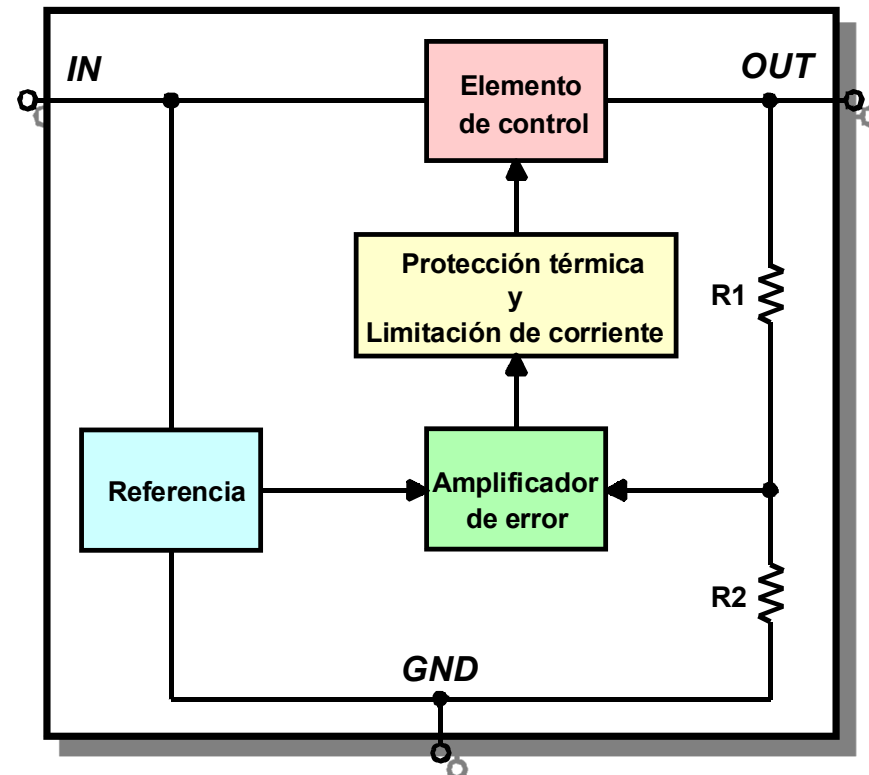
### Linear basic regulator with additional elements:


- Limitation of the maximum output current as a function of the difference in input-output voltage → power limitation.
- Thermic protection → the control element can be disconnected.
- Error amplifier internally compensated
- Reference voltage of low noise and high stability.



# 6. Integrated Power Supplies
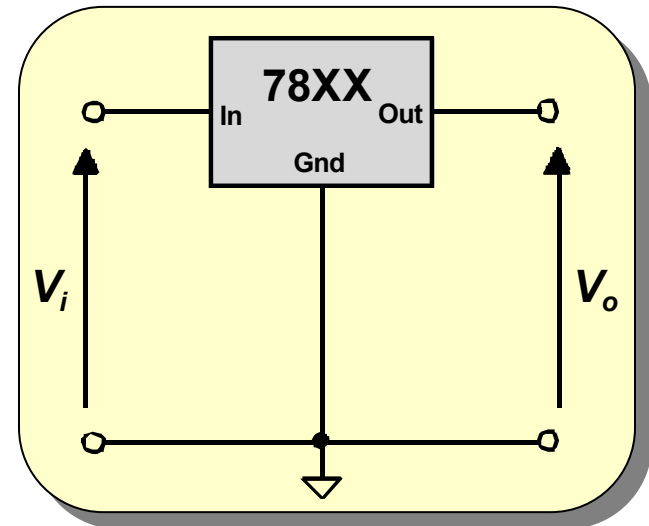
## Regulators of 3 terminals. Positive.

- No external element is needed.
- The input is provided by a non-stabilized voltage supply or by a DC supply.
- The input voltage must be higher than the output, at least 2 or 3V.




# 6. Integrated Power Supplies

## Regulators of 3 terminals. Positive.

➤ External elements can be added:

Protection against C2 discharge if  $V_i$  decreases or becomes zero

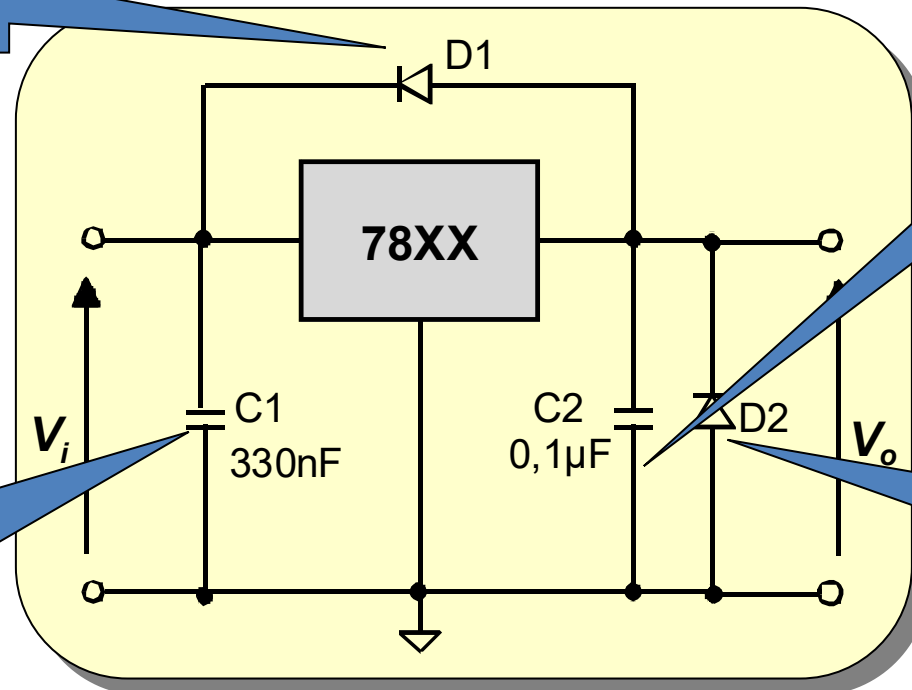Only necessary if the regulator is far away from the non-regulated supply




Improves the transient response of the regulator

Protection against polarity inversions in the output

# 6. Integrated Power Supplies

## Regulators of 3 terminals. Positive.

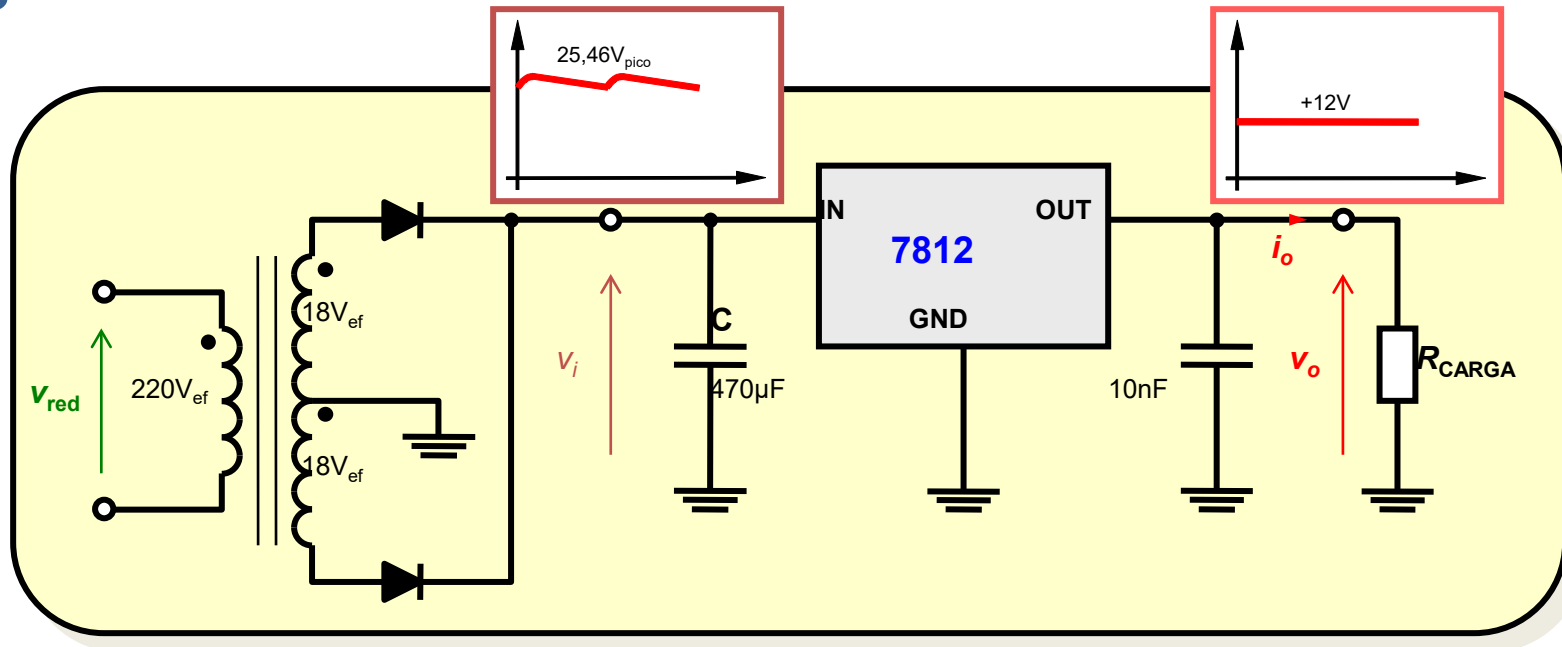


- The selection of  $N2:N1$  is important to minimize the power dissipation.
- The capacitor  $C$  assures that  $v_i$  never decreases under a specific value.
  - The discharge or output current is  $i_o$ .

# 6. Integrated Power Supplies

## Regulators of 3 terminals. Negative.
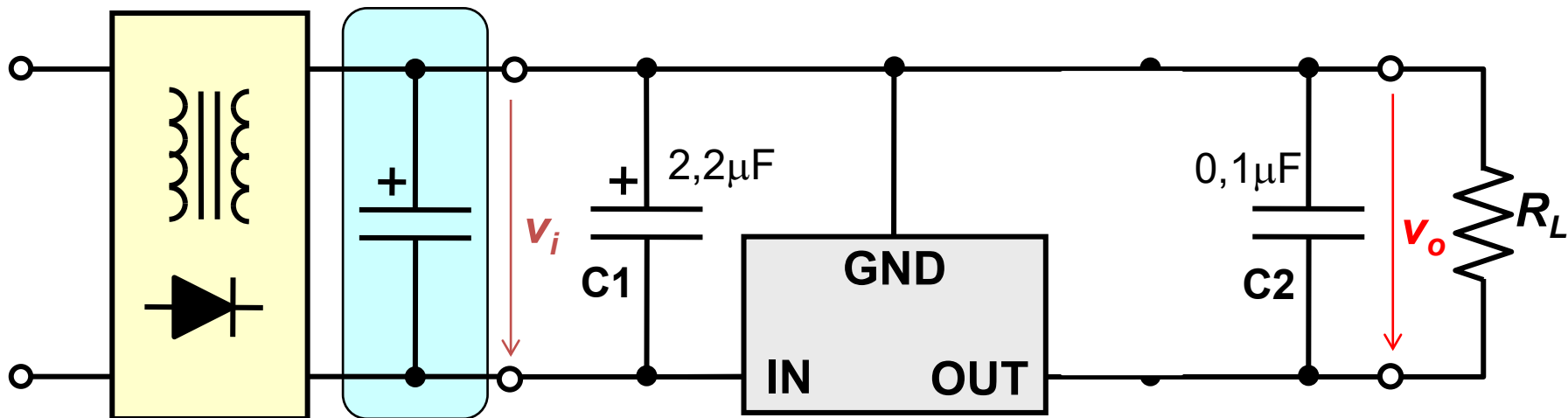
### ➤ Series 79XX.

- Similar to the positive regulators 78XX.
- The capacitor in the output assures the stability.
- As in 78XX, C1 is only necessary if the regulator is far away from the filter. C3 improves the transient response.
- All capacitors associated to the regulator should be connected as near as possible from the regulator.







# 6. Integrated Power Supplies
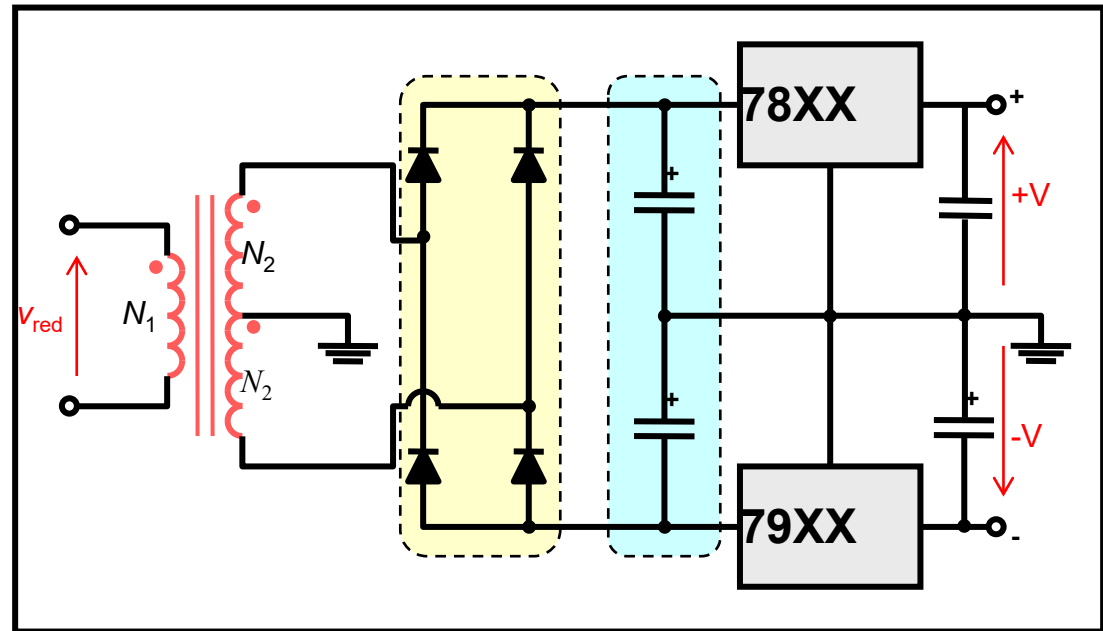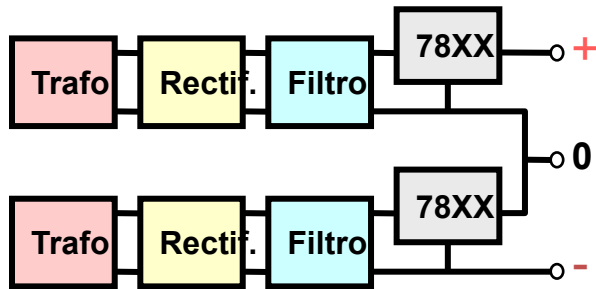
## Regulators of 3 terminals.

- They simplify the implementation of symmetric supply sources.


This could be achieved with 2 different 78XX, but 2 complete supply sources would be needed:



Using 79XX the design is simpler

# 6. Integrated Power Supplies

## Regulators of 3 terminals.

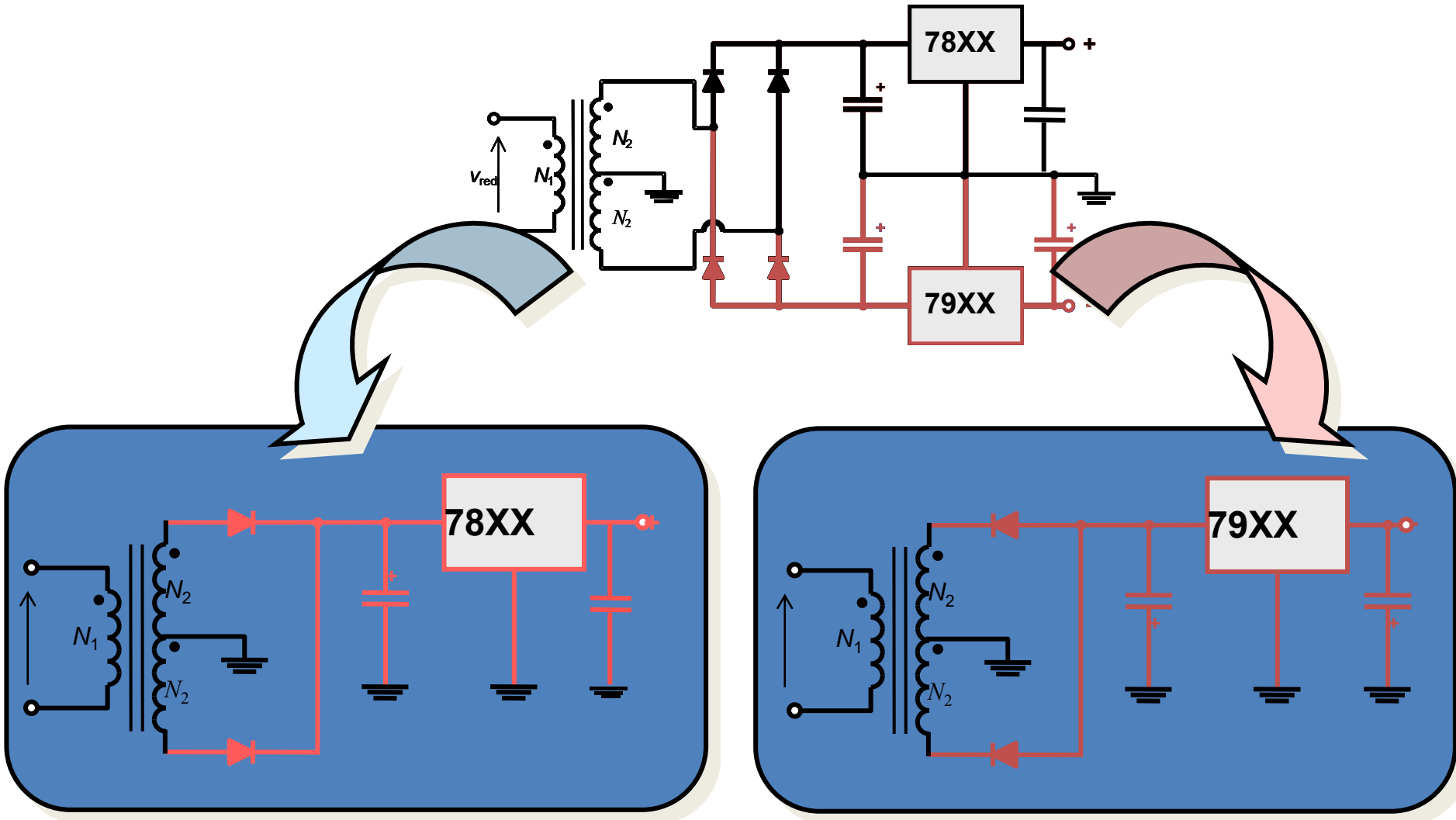

# 6. Integrated Power Supplies

## Regulators of 3 terminals. Increase of the output current.


51

### ➤ Addition of a transistor and a resistor to increase the output current.

- Transistor → supports most of the current supplied to the load.
- Regulator → assures the stability of the output voltage.
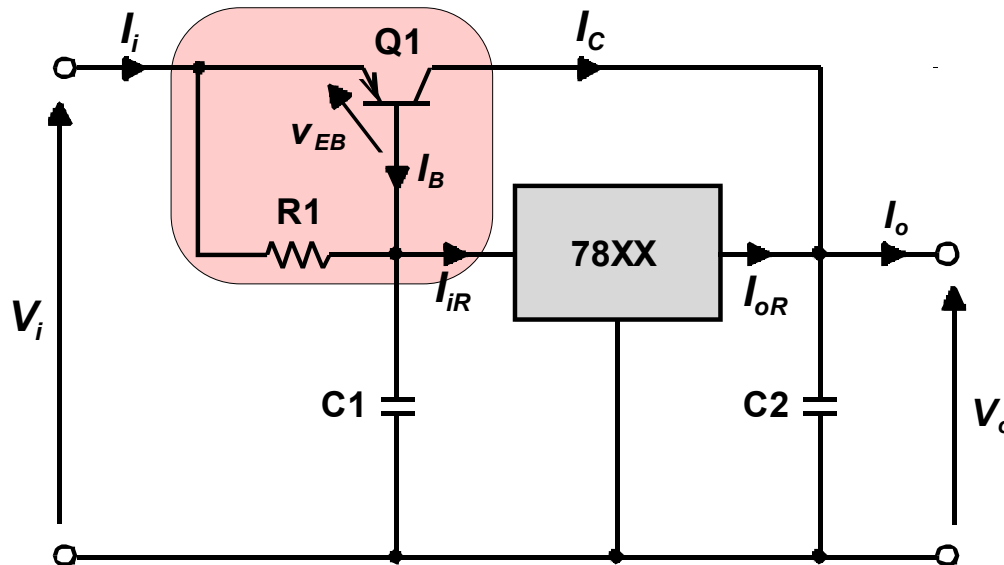
### ➤ The minimum difference of input-output voltage increases.

- $V_{EB}$  + minimum voltage drop in the regulator (2 or 3 V).




$$R_1 = \frac{V_{EB}}{I_{iR} - \frac{I_C}{\beta}}$$

$$I_o = I_{oR} + I_C$$


# 6. Integrated Power Supplies
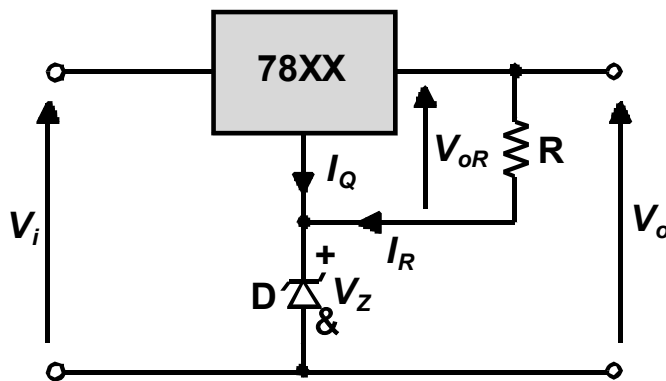
## Regulators of 3 terminals. Increase of the output voltage.

- With a fixed regulator a different output voltage (from the nominal one) can also be obtained.
- Addition of a positive voltage to the reference terminal (Gnd/Common) of the regulator.
  - The quiescent current (8.5 mA maximum) must be assured.



$$V_o = V_{oR} + V_Z$$

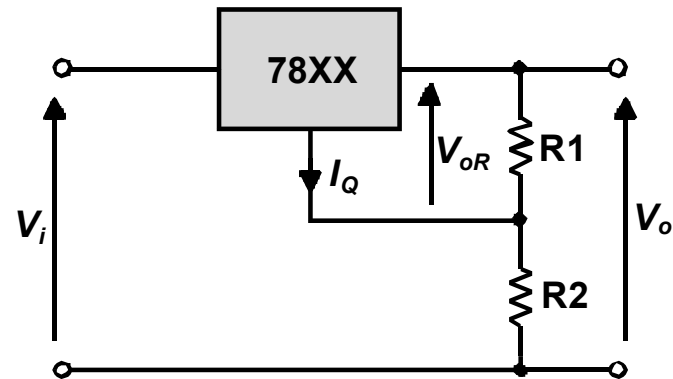


$$V_o = V_{oR} \left( 1 + \frac{R_2}{R_1} \right) + I_Q \cdot R_2$$

# 6. Integrated Power Supplies

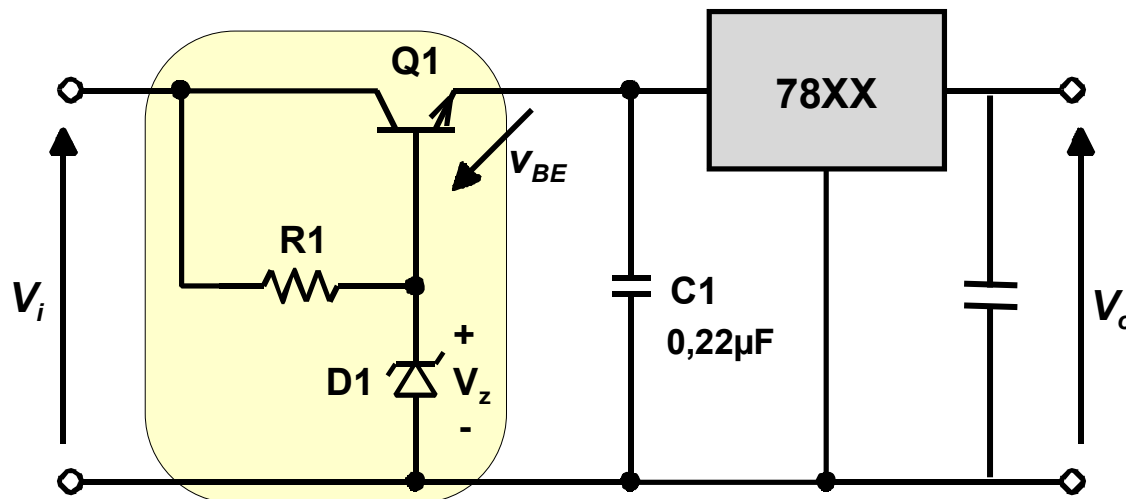
## Regulators of 3 terminals. Elevated input voltages.

- In general, the maximum input voltage for a 78XX is 35 V (for 79XX, -35 V).
- If the input voltage is higher, a stabilizer can be connected before the regulator.
- This solution helps to dissipate less power in the regulator.



# 6. Integrated Power Supplies


## Voltage Converters: ICL7660

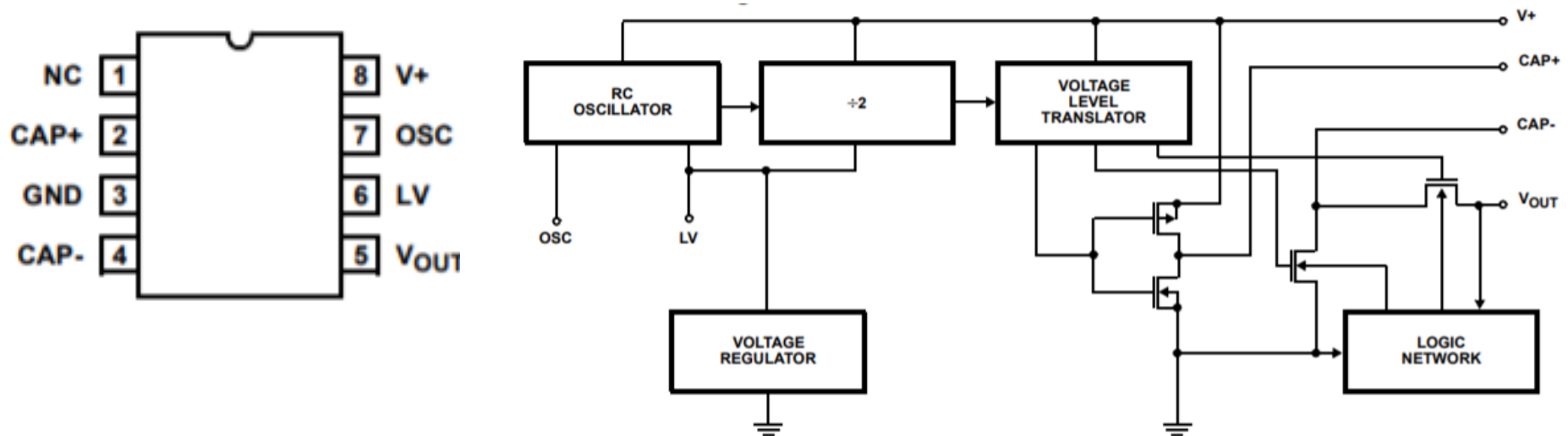


- CMOS power supply circuits
- Supply voltage conversions:  
 $+1.5\text{V to }+10.0\text{V}$  ➔  $-1.5\text{V to }-10.0\text{V}$ .
- Voltage doublers

# 6. Integrated Power Supplies
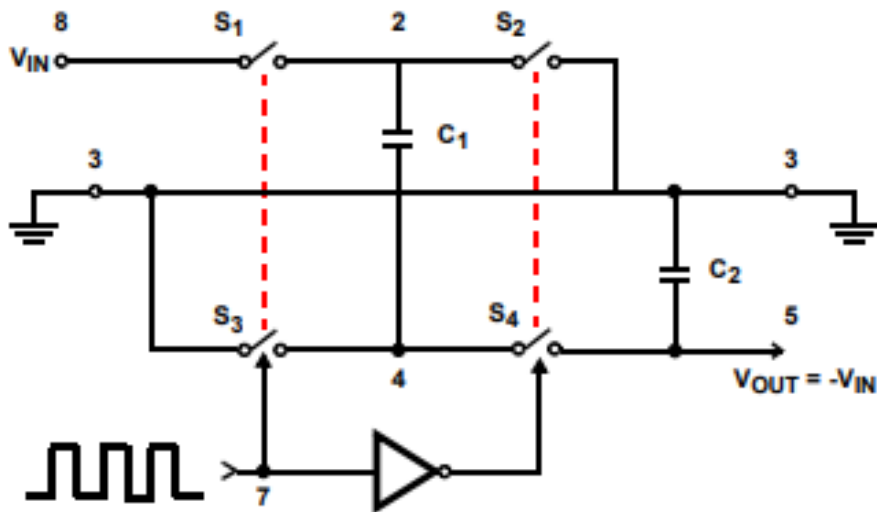
## Voltage Converters: ICL7660 as negative converter



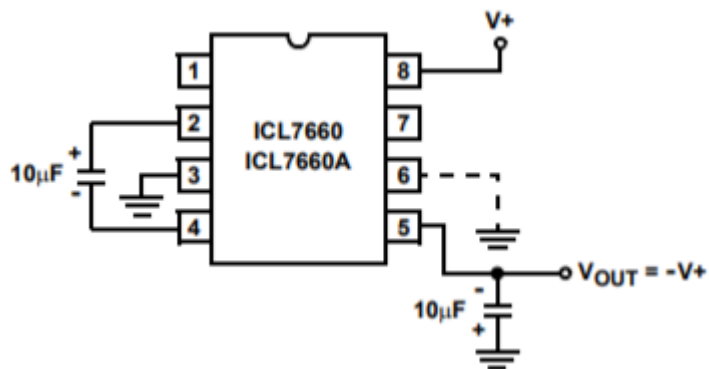
CMOS Switches:  
 S1, S3 charge of C1 to  $V_{in}$   
 S2, S4  $V_{out} = -V_{in}$



Simple negative converter  
 Pin 6 to ground only if  $V+ < 3.5V$

# 6. Integrated Power Supplies
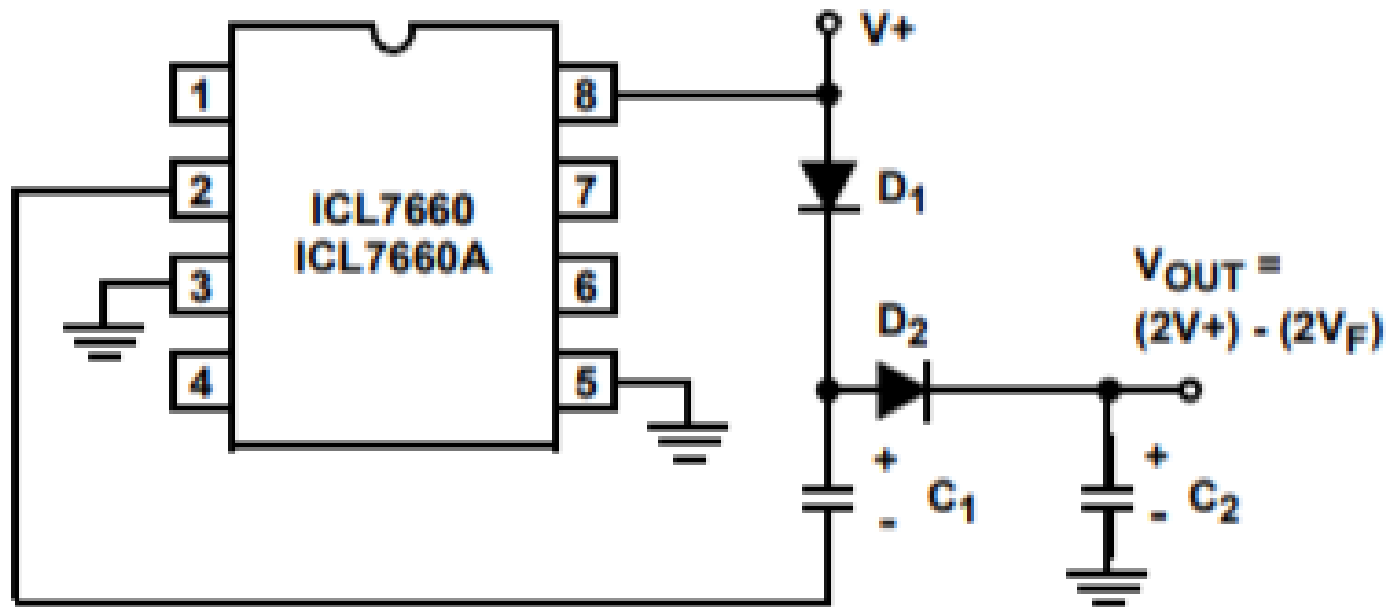
## Voltage Converters: ICL7660 as voltage doubler




$V_F$  forward voltage of the diode




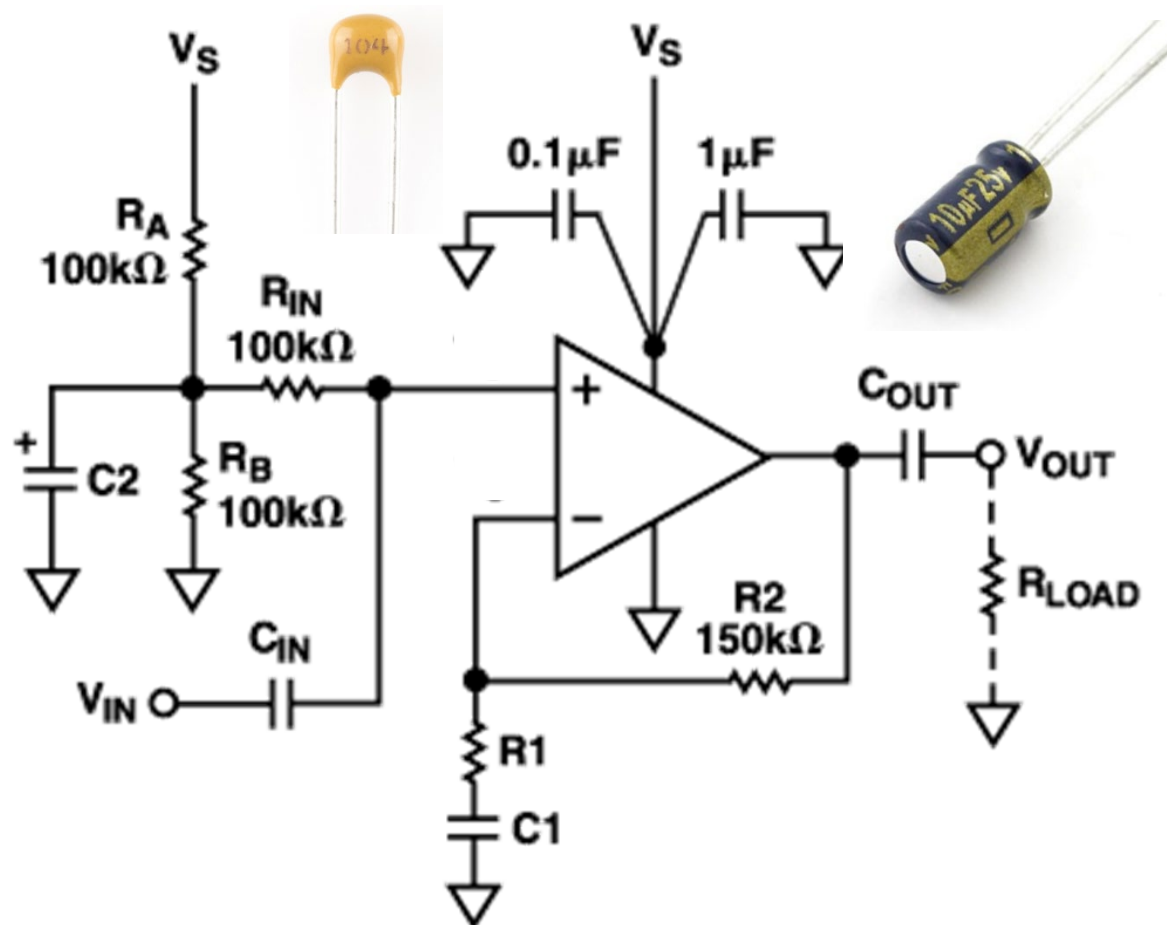
# 7. Decoupling capacitors

They operate as charge reservoir (decoupling)



# 7. Decoupling capacitors

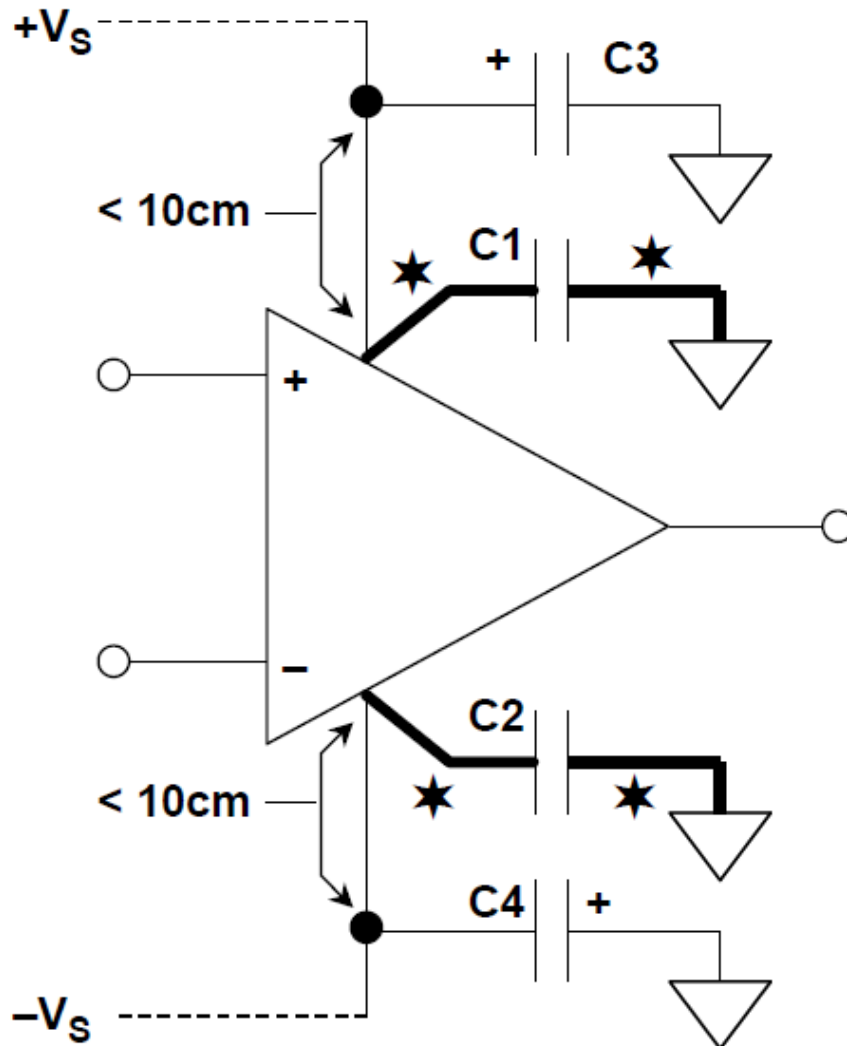

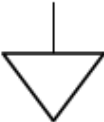 = LARGE AREA GROUND PLANE

 = LEAD LENGTH MINIMUM



C1, C2: LOCALIZED **HF** DECOUPLING, LOW INDUCTANCE CERAMIC,  $0.1\mu\text{F}$

C3, C4: SHARED **LF** DECOUPLING, ELECTROLYTIC, 10 TO  $50\mu\text{F}$



# 8. Non-symmetrical supply

Work out the voltage range at the output  $V_{OUT}$

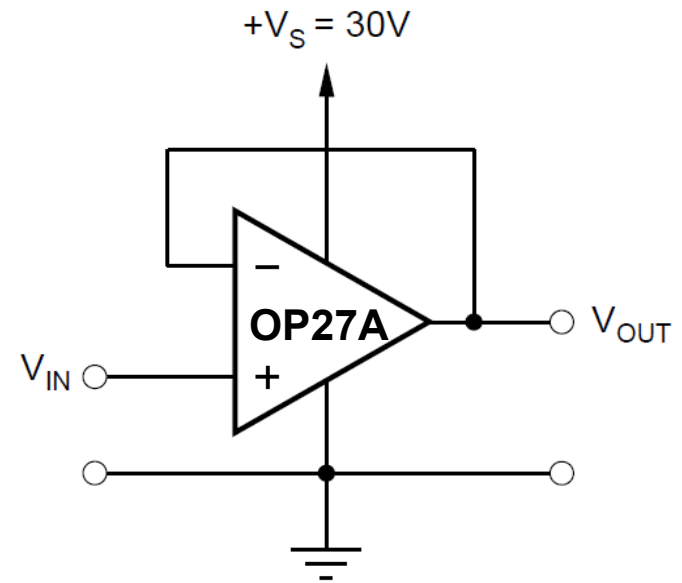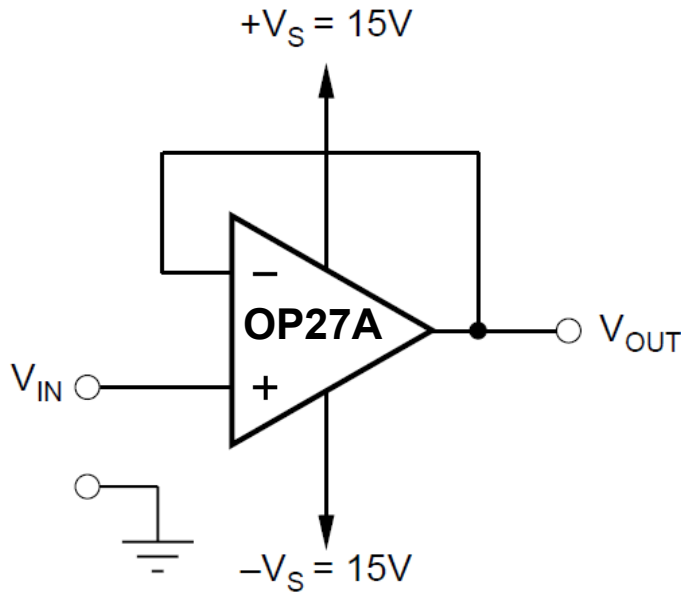

**OP27**

## SPECIFICATIONS

### ELECTRICAL CHARACTERISTICS

$V_S = \pm 15\text{ V}$ ,  $T_A = 25^\circ\text{C}$ , unless otherwise noted.

Data Sheet

Parameter	Symbol	Test Conditions	OP27A/OP27E			OP27G			Unit
			Min	Typ	Max	Min	Typ	Max	
OUTPUT VOLTAGE SWING	$V_o$	$R_L \geq 2\text{ k}\Omega$	$\pm 12.0$	$\pm 13.8$		$\pm 11.5$	$\pm 13.5$		V
		$R_L \geq 600\ \Omega$	$\pm 10.0$	$\pm 11.5$		$\pm 10.0$	$\pm 11.5$		V


# 8. Non-symmetrical supply

Work out the symmetrical input voltage range can process the circuit (typically).

$R_L = 100\text{ k}\Omega$

Work out the range for  $V_{OUT}$

(floating ground)

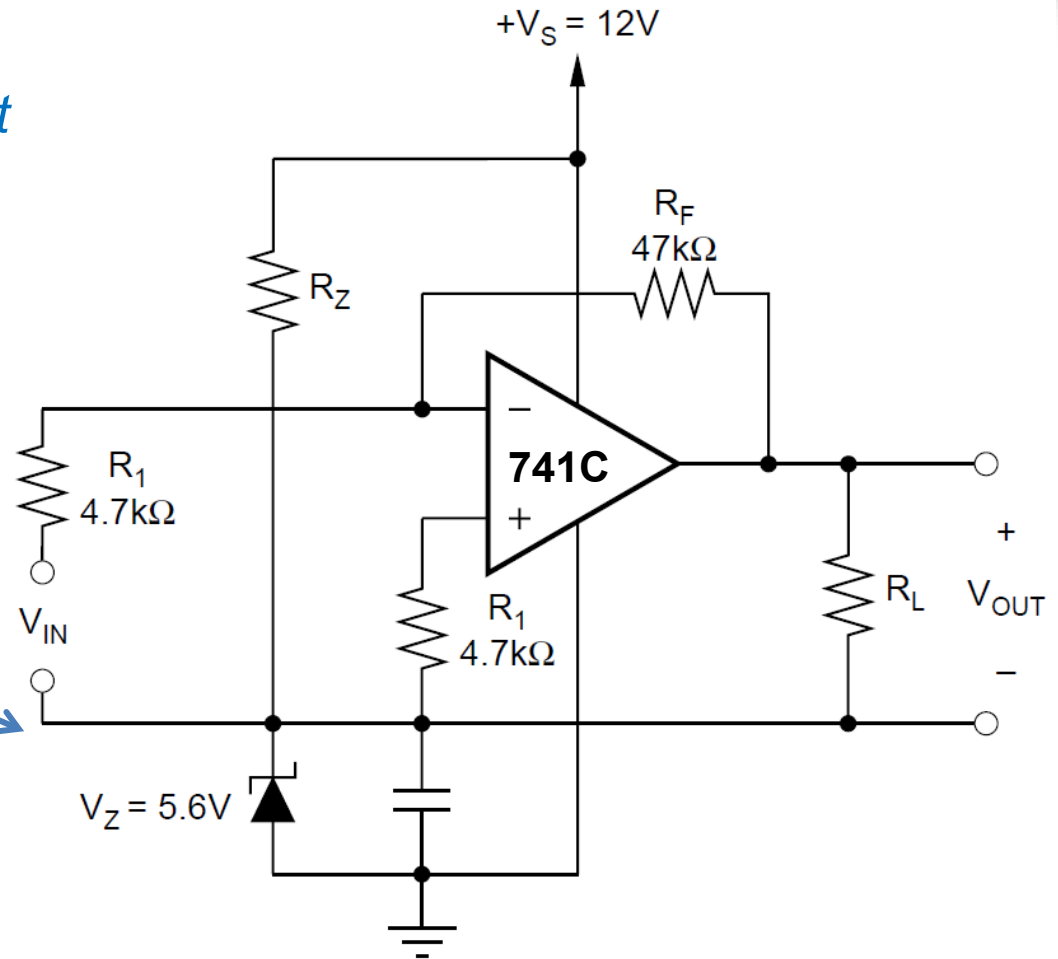

Electrical Characteristics, LM741C

PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNIT
Output voltage swing	$V_S = \pm 15\text{ V}$	$R_L \geq 10\text{ k}\Omega$	$\pm 12$	$\pm 14$	V
		$R_L \geq 2\text{ k}\Omega$	$\pm 10$	$\pm 13$	


# 8. Non-symmetrical supply

Work out the symmetrical input voltage range can process the circuit (typically).

$$R_L = 100 \text{ k}\Omega$$


Work out the range for  $V_{OUT}$

Work out the current in the zener diode

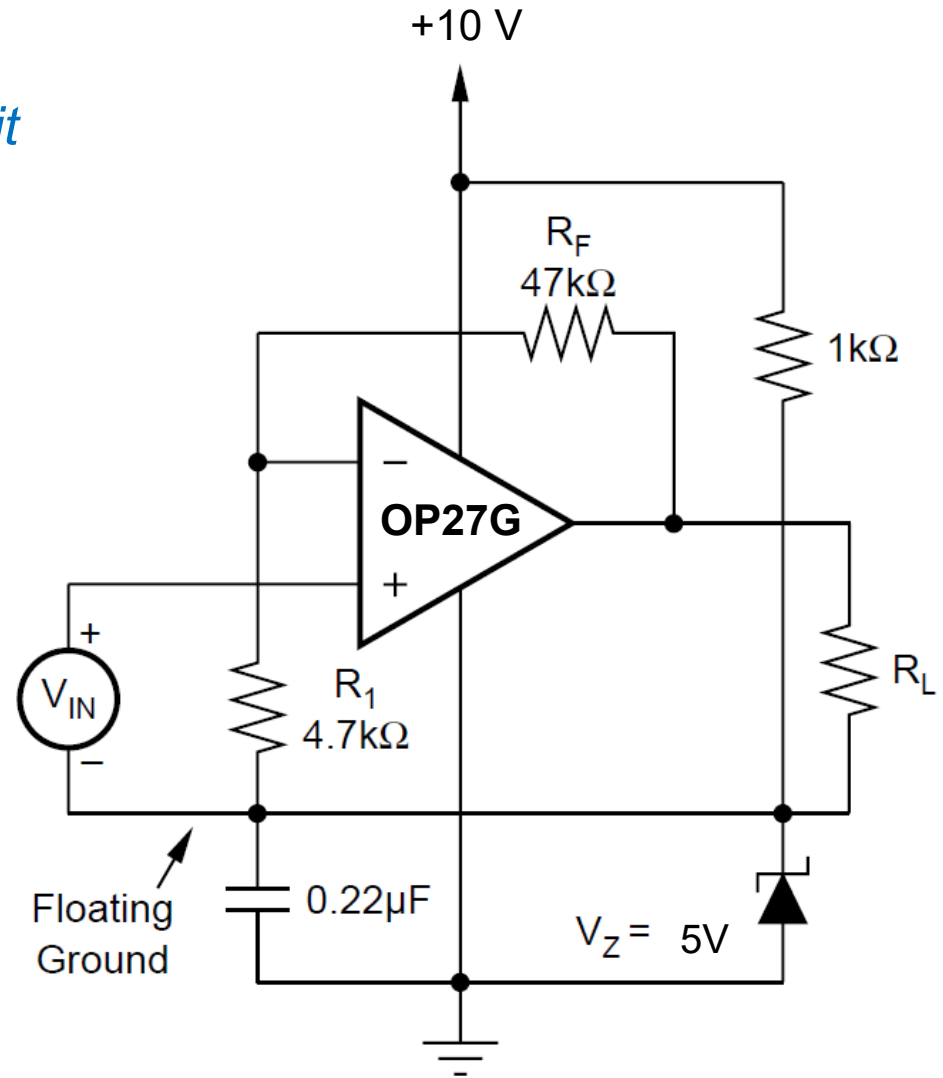
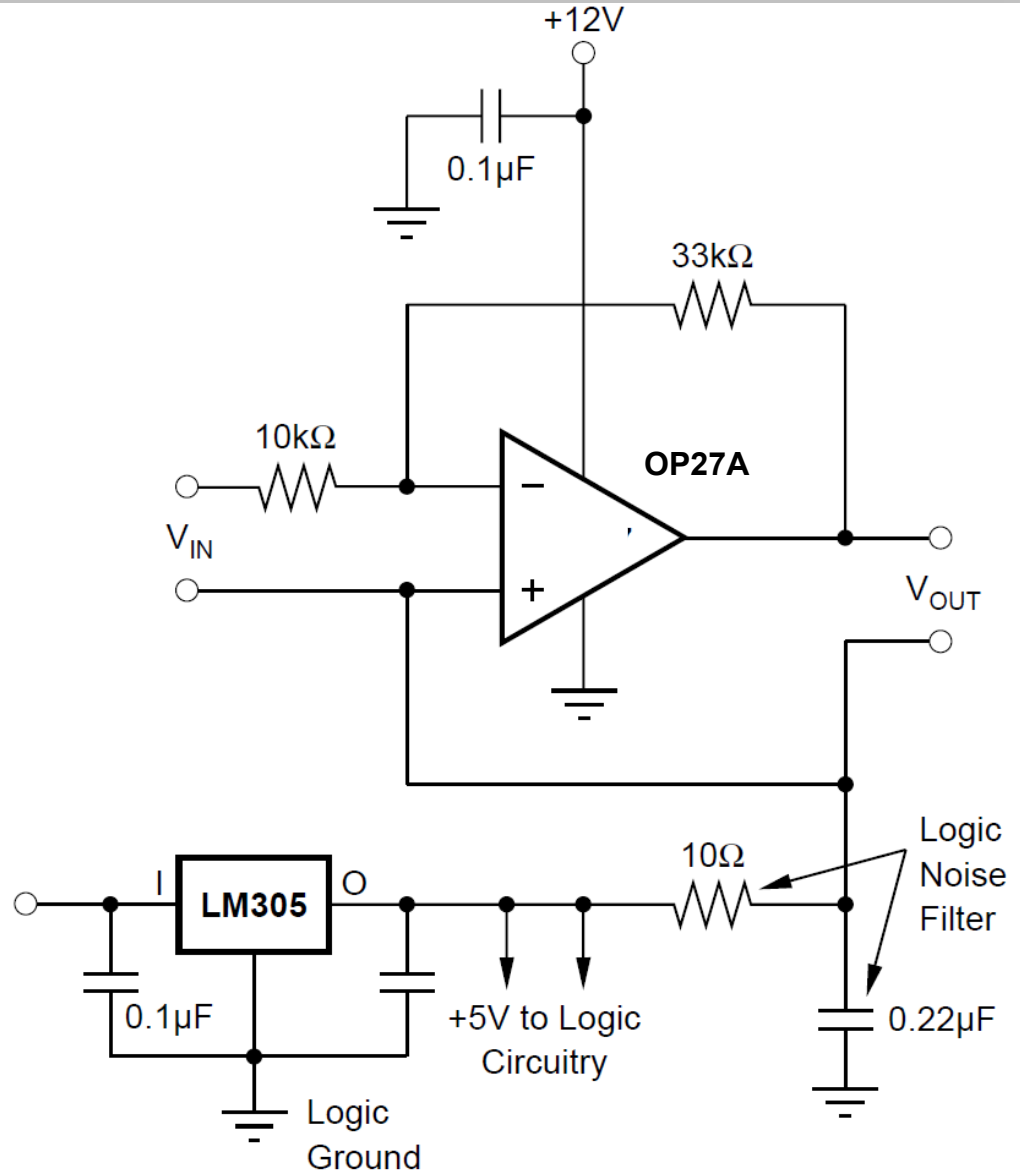
# 8. Non-symmetrical supply

*Estimate the gain of the system ( $V_{OUT}/V_{IN}$ ) and the maximum range at the input (typical values)*




# 8. Non-symmetrical supply

The OA supply is +15 V, work out the voltage at the output of the OA.


What is the role of  $C_{IN}$ ,  $C_1$  and  $C_O$ ?

(coupling capacitors, DC biasing)

Work out the range of  $V_{IN}$

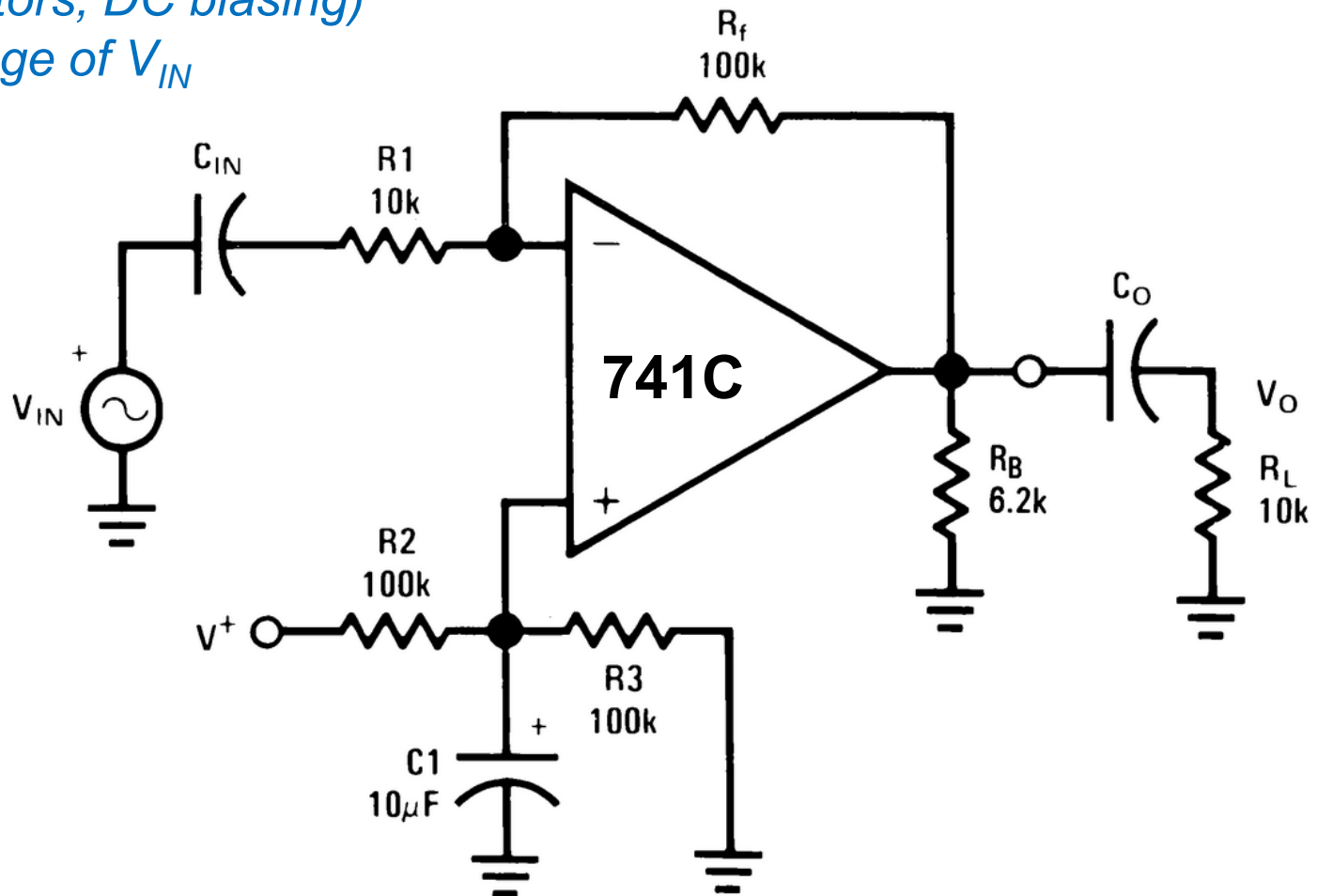

# 9. Consumption estimation

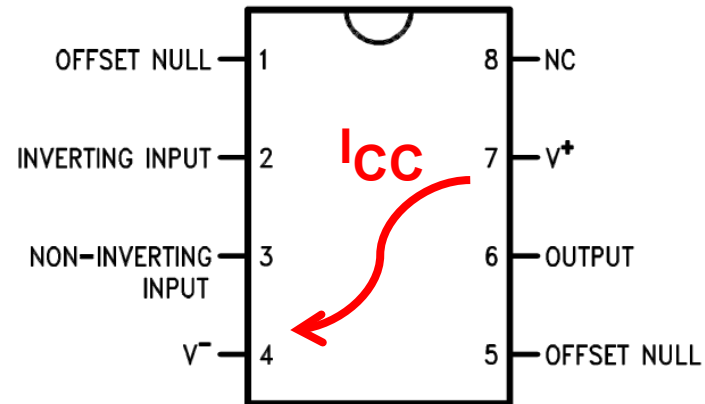

## Absolute Maximum Ratings


		MIN	MAX	UNIT
Supply voltage	LM741, LM741A		±22	V
	LM741C		±18	
Power dissipation <sup>(4)</sup>			500	mW

## Electrical Characteristics, LM741C

PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNIT
Supply current	$T_A = 25^\circ\text{C}$		1.7	2.8	mA
Power consumption	$V_S = \pm 15\text{ V}, T_A = 25^\circ\text{C}$		50	85	mW



# 9. Consumption estimation

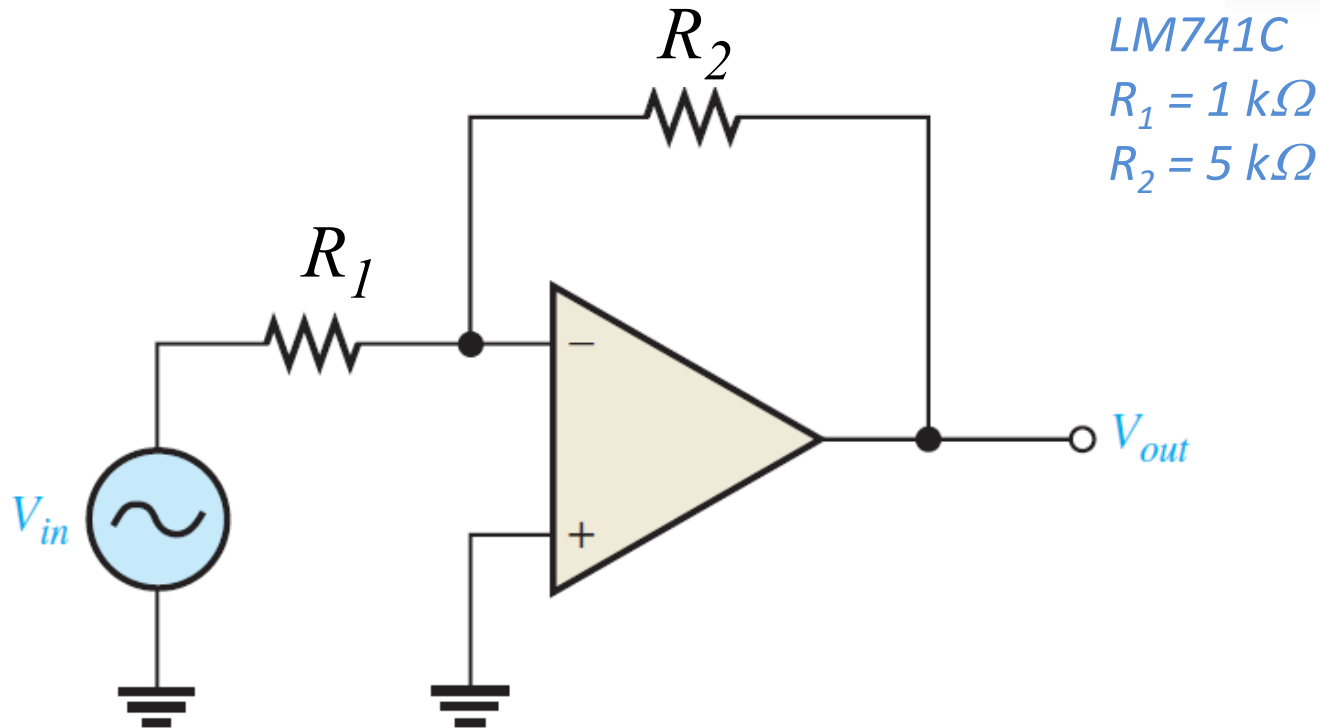

*Estimate the current supplied by each supply source when the OA is supplied with  $\pm 15\text{ V}$  and  $V_{in} = +2\text{ V}$*

*Estimate the power dissipated by the OA. Is the maximum power exceeded?*

*Repeat the calculations when the supply is  $+30\text{ V}$  and  $V_{in} = -2\text{ V}$*

# 9. Consumption estimation

If the input voltage  $V_e$  varies between  $\pm 1$  V, estimate:


- 1) Maximum current consumption (provided by the supply source)
- 2) Maximum power dissipated by the OA. Check that the maximum power is not exceeded.

AO 741C ( $\pm 15$  V)

$R_1 = 1$  k $\Omega$

$R_2 = 9$  k $\Omega$

$R_L = 5$  k $\Omega$

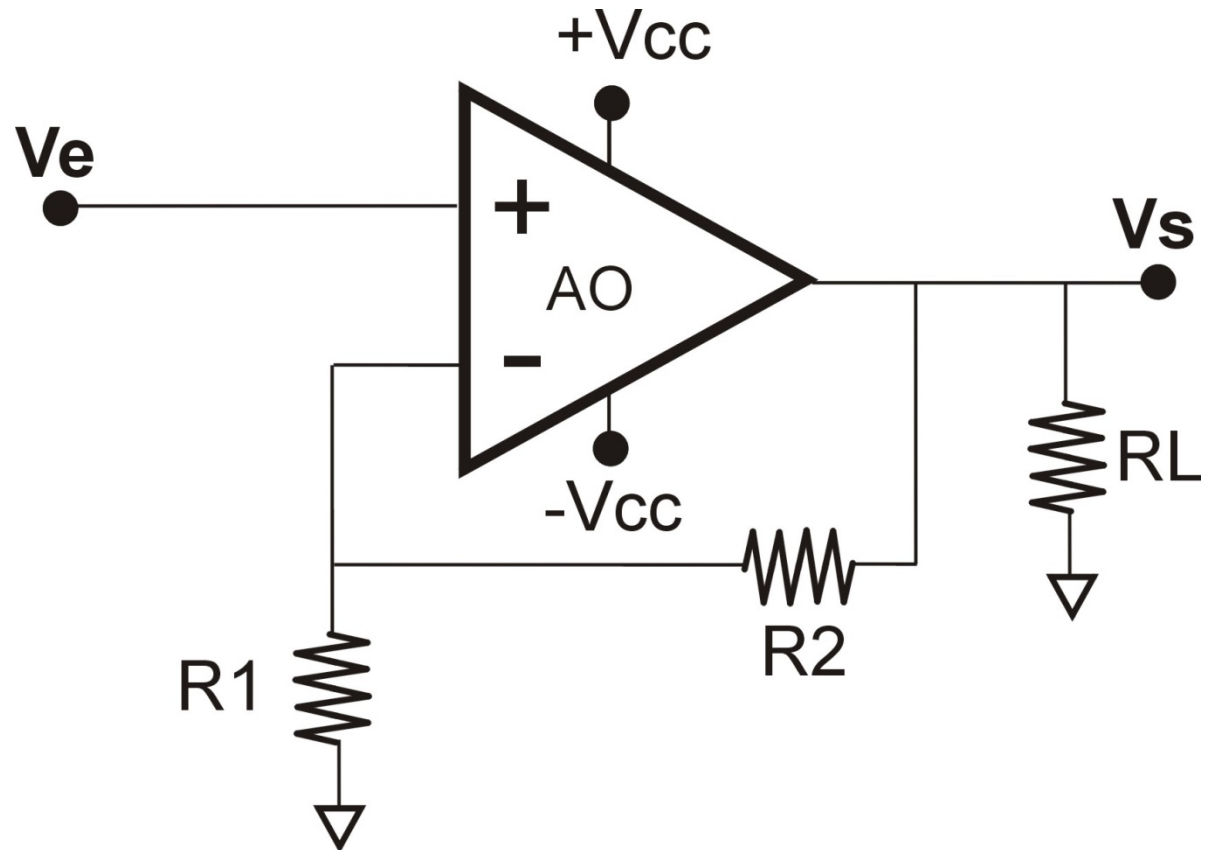

# 9. Consumption estimation

If the input voltage  $V_e = -2\text{ V}$ , estimate:

- 1) Maximum current consumption (provided by the supply source)
- 2) Maximum power dissipated by the OA. Check that the maximum power is not exceeded.
- 3) Check that the balance of dissipated powers and provided by all the components of the circuit.

AO 741C (+30 V)

$R1 = 2.2\text{ k}\Omega$

$R2 = 11\text{ k}\Omega$

